


CX1005

Digital Logic

Sequential Circuits

Review of Combinational Circuits

 - So far, we have investigated *combinational* circuits
- The output of a combinational circuit is purely a function of the present inputs to it
 - *output = f(input)*
- When the inputs are changed, the output will change to that determined by those inputs (after a short propagation delay)
- Knowing only the *current* inputs, we can always determine the output





Combinational and Sequential


- *Sequential* circuits introduce the idea of *state*
 - The state of a circuit encodes sufficient information about the past to determine how it will react with inputs to produce an output
- The output of a sequential circuit depends on **both** the *current* inputs and *previous* inputs
- In this sense, *sequential circuits have memory*, whereas combinational circuits have no memory.

Sequential Logic

  
- We'd like to store a single bit
- Flight attendant call button
 - Press “Call”: light on
 - Stays on after button released
 - Press “Cancel”: light off
 - Stays off after button released
 - Can we use a gate?



1. Call button pressed – light turns on

 


 
2. Call button released – light **stays on**



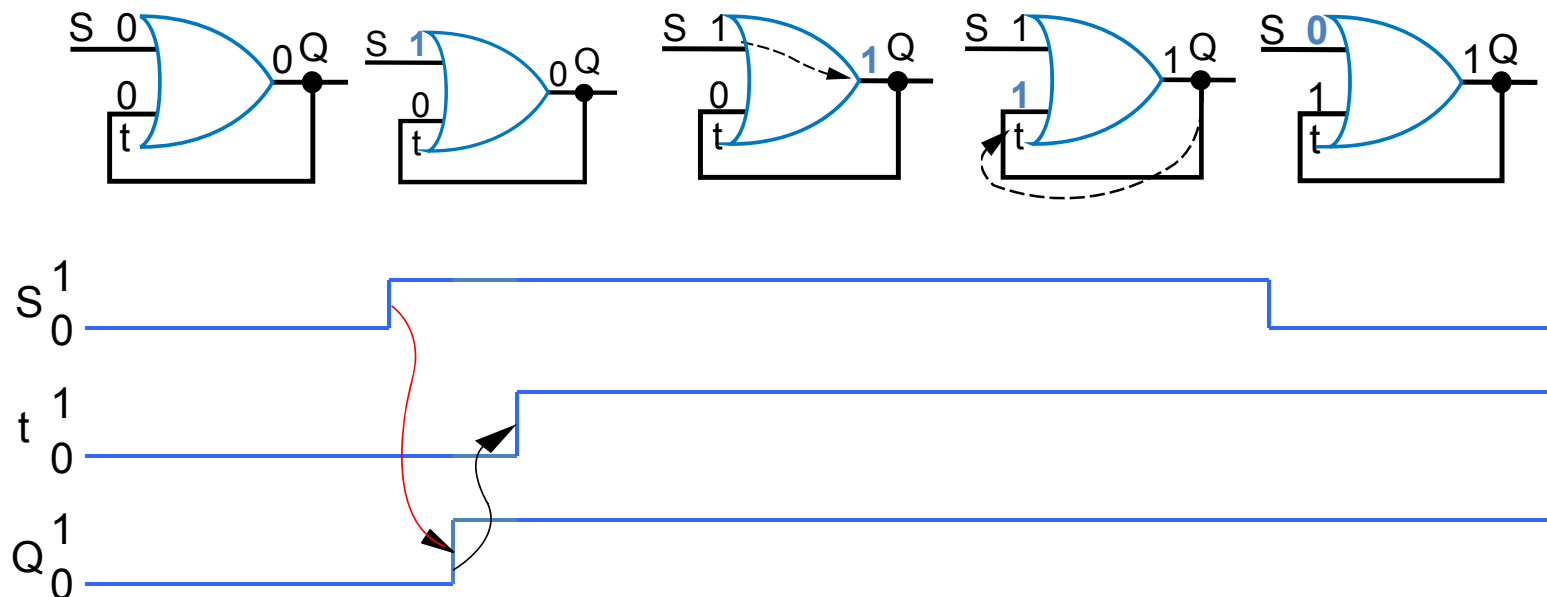 3. Cancel button pressed – light turns off




Sequential Logic

- What if we add feedback?
 - S will now cause 1 to be stored




Set-Reset (SR) Latch

 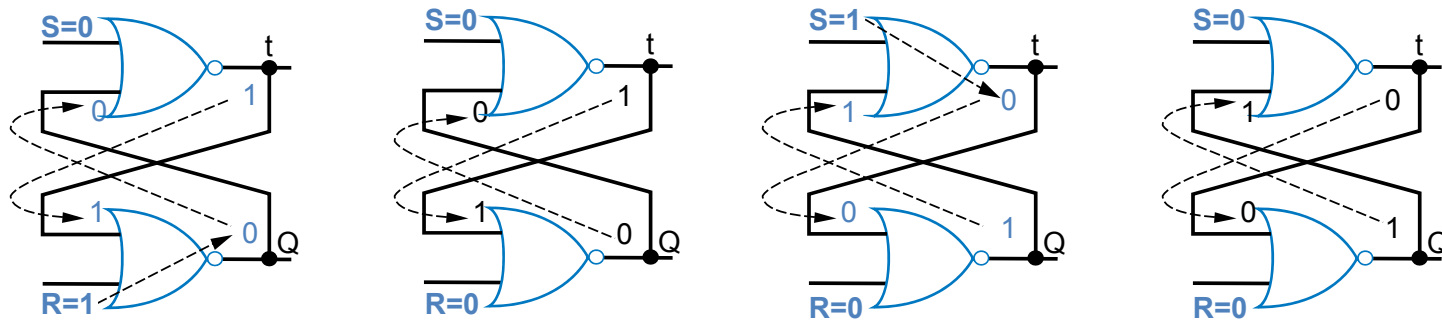 - The most basic circuit for storing a bit is the *SR latch*:




Set-Reset (SR) Latch

 - The SR latch allows us to implement the flight attendant call system easily
 - Connect “call” to S, and “cancel” to R
 - Q stays at 1 even after “call is released”



Set-Reset (SR) Latch

 
- There is, though, a problem with the SR Latch
- What happens when both S and R are asserted?




- When both S and R is then de-asserted at the same time, we may get oscillation at the output:
 - Constant swapping from 0 to 1 to 0 ...
- Normally, one gate is a little faster so output will eventually stabilize, but which?
 - Impossible to know

Set-Reset (SR) Latch

 - Maybe the designer can stop the problem of both S and R being 1






 - The problem is, signals take time to travel through gates, so call to R is longer than call to S



Gated/Enabled SR Latch

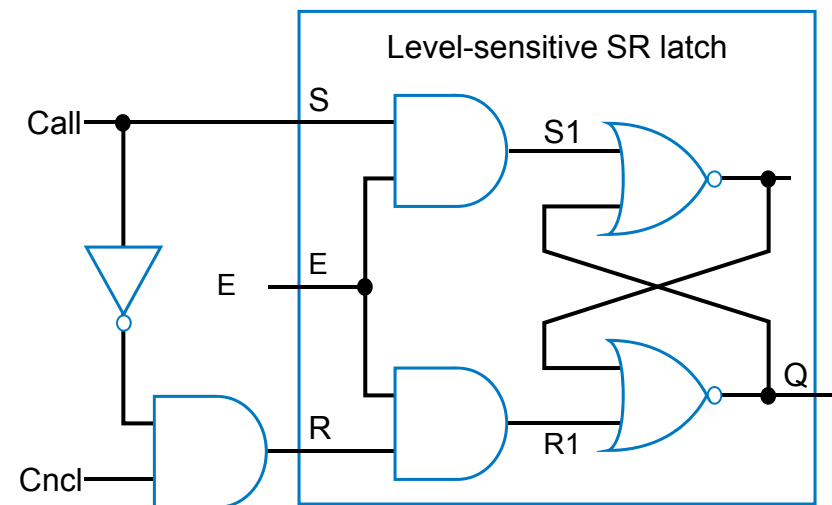  
- The *enabled SR latch* will only respond to inputs when E is high – *level-sensitive*
- Can now ensure S and R never both high when E high – glitches unimportant



SR Latches


- We can capture the behavior of the above latches using a truth table:

 - Q means the current state
- Q+ means the next state



SR Latch

S	R	Q+	Function
0	0	Q	Store
0	1	0	Reset
1	0	1	Set
1	1	?	Undefined

 


Enabled SR Latch


E	S	R	Q+	Function
0	X	X	Q	Store
1	0	0	Q	Store
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	?	Undefined

Transparent D Latch

 - The D latch, also called the transparent latch
- Removes the possibility of invalid inputs
 - Inverter ensures R is always opposite of S
 - A single input controls both states of the latch



E	S	R	Q+	Function
0	X	X	Q	Store
1	0	0	Q	Store
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	?	Undefined


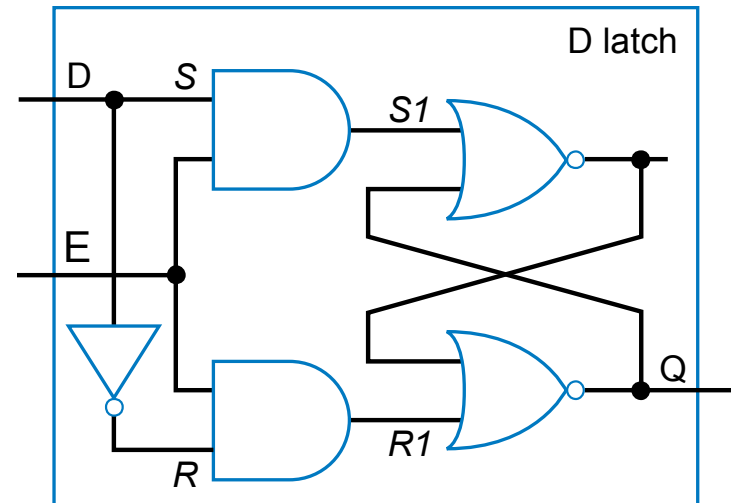


E	D	Q+
0	X	Q
1	0	0
1	1	1

Transparent D Latch

- The D latch effectively passes its input through to its output whenever the enable input is high
- Hence, “transparent”
- If enable is low, the output is held
- Truth table for a D latch:



E	D	Q+	Function
0	X	Q	Store
1	0	0	Transparent
1	1	1	Transparent

 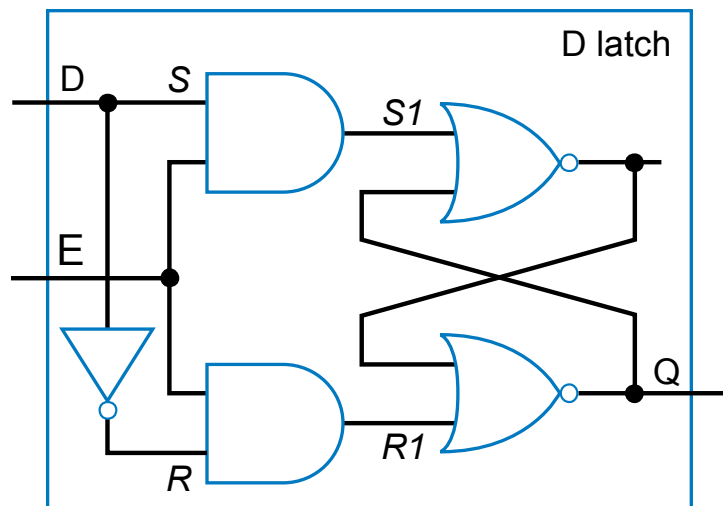

Transparent D Latch

- The D latch effectively passes its input through to its output whenever the enable input is high
- Hence, “transparent”
- If enable is low, the output is held
- Truth table for a D latch:


E	D	Q+	Function
0	X	Q	Store
1	0	0	Transparent
1	1	1	Transparent

 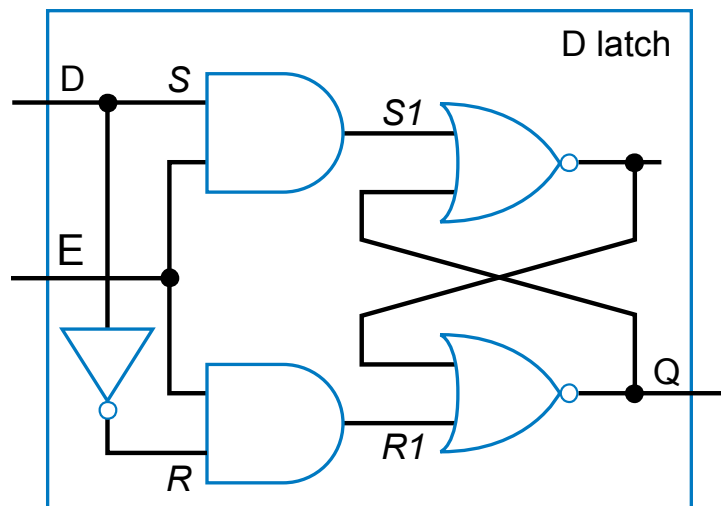


Active-Low Latches

- Note that it's possible to create active-low versions of the latches previously shown
- Swap the **nor** for **nand** and the **or** for **and**:

Active-Low SR Latch

 

Active-Low Transparent Latch

 


E	D	Q+	Function
1	X	Q	Store
0	0	0	Transparent
0	1	1	Transparent

Timing in Circuits

- So far, we have assumed that inputs cause a change in the output of a gate immediately
- The reality is it takes a short amount of time
- We call this the **propagation delay**
- This is the time it takes for a change at the input to create the requisite change at the output
- We can work out the propagation delay through a circuit by summing the propagation delays of the individual gates

Timing in Circuits

 - Assume an **and** gate has a delay of 4ns and an **inverter** has a delay of 2ns:




Timing in Circuits

- The propagation delay, t_p , may differ between different inputs and outputs in the same circuit
- Hence we can give the propagation delay for each input-output pair:
 - a input to f output $t_p = 10\text{ns}$
 - b input to f output $t_p = 8\text{ns}$
- If we report a single number, we always use the worst (i.e. longest path)

The Clock

 
- In digital systems, sequential components are connected to what we call a “clock”
- The clock is a signal that continuously toggles between 0 and 1 at a fixed rate:



- It is called a clock because it oscillates much like the “tick-tock” of a clock
- This is where the MHz and GHz numbers for chips come from – how fast does the clock oscillate?

The Clock

 - The **period** of the clock is the time it takes to complete **one complete cycle** – we call this a cycle




- The **frequency** is the inverse of the period:
 - 10ns period = $10 \times 10^{-9} \text{s}$, $1/10 \times 10^{-9} = 10^8 \text{Hz} = 100 \text{MHz}$
 - 1ns period = $1 \times 10^{-9} \text{s}$, $1/1 \times 10^{-9} = 10^9 \text{Hz} = 1 \text{GHz}$
 - 4ns period = $4 \times 10^{-9} \text{s}$, $1/4 \times 10^{-9} = 2.5 \times 10^8 \text{Hz} = 250 \text{MHz}$

Timing of Latches

Truth table of a D Latch


E	D	Q+	Function
0	X	Q	Store
1	0	0	Transparent
1	1	1	Transparent

- Consider a chain of latches:

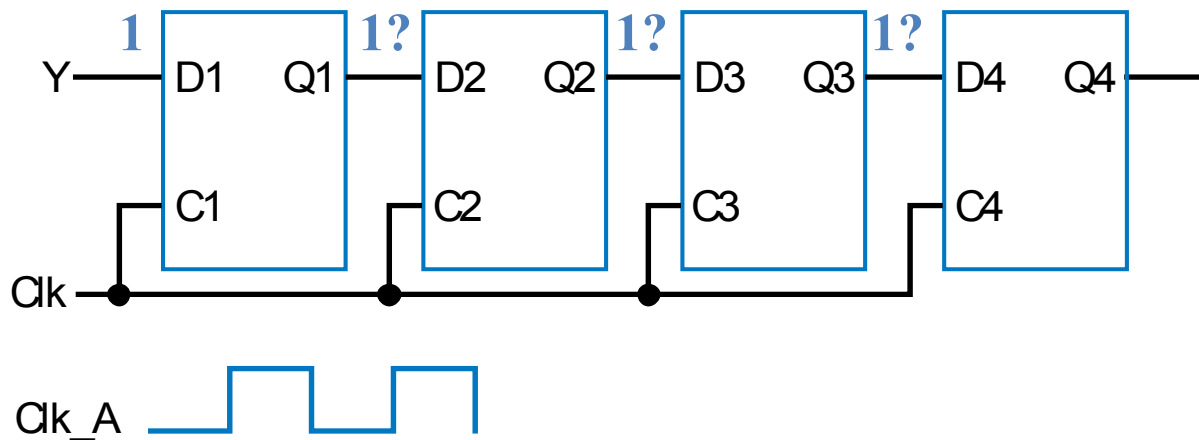


- When Clk_A is 1, how many latches will the input pass through?
- With Clk_A, it may be more, Clk_B, fewer

Timing of Latches

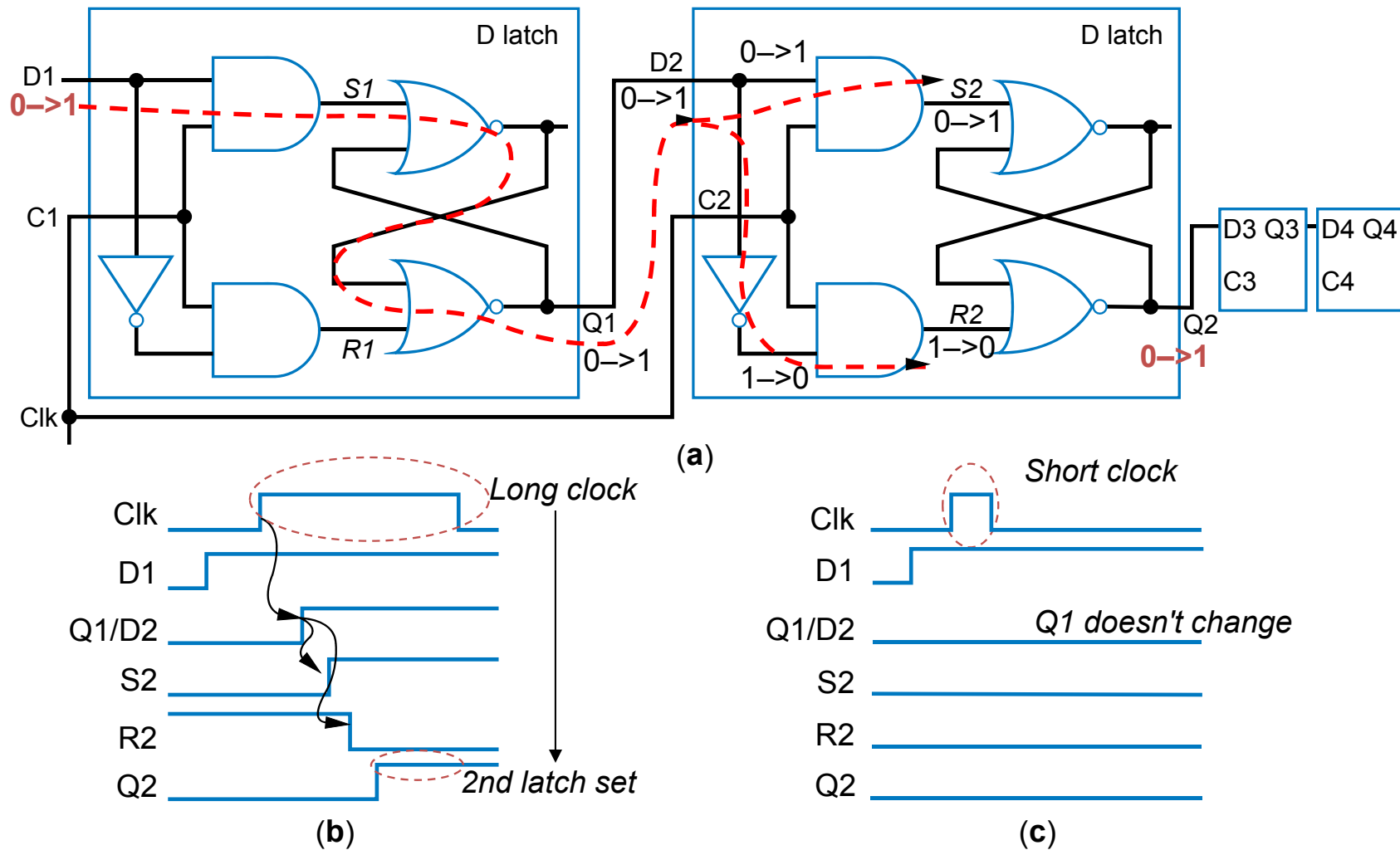

Edge Triggered Flip-Flops

 - We can use an edge triggered flip-flop to overcome the limitation of D latches
- At each clock rising edge each flip flop will take its D input and produce that value on its Q output
- How do we implement an edge triggered flip flop?




Edge-Triggered Flip-Flops

- Master-Slave implies two latch stages:
 - Master stage is enabled when control is low, and samples the current input, while slave is disabled, locking it in the middle
 - When control goes high, the master is disabled, and the slave uses the value from the middle to determine its output
 - Hence, the only time an output will change is at the rising edge
 - For a negative-edge triggered setup, the master responds to high enable, and the slave to low enable


Edge-Triggered Flip-Flops

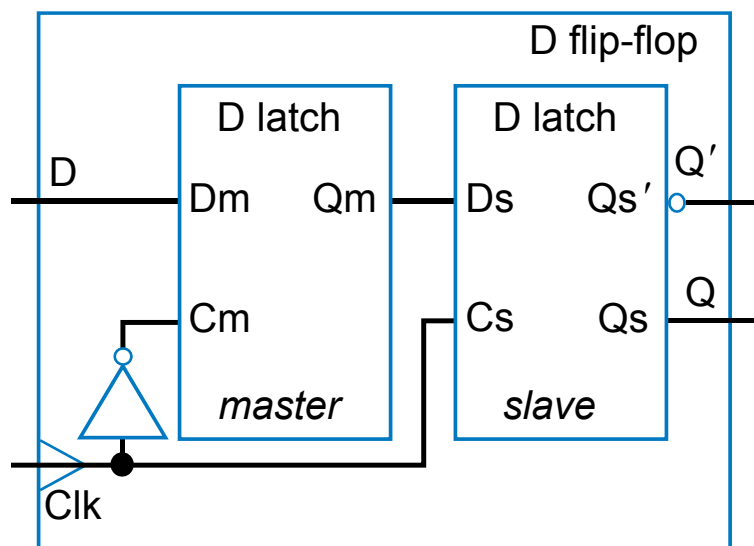- The master and slave are each just a D latch:




Truth table of a D Latch

E	D	Q+	Function
0	X	Q	Store
1	0	0	Transparent
1	1	1	Transparent

 

Edge-Triggered Flip-Flops

 
- Rather than invert the clock as in the last slide, we can use an active low version (more correct)
- Example design of D flip-flop:



- Note that there are many possible designs, and many are more compact than above

Edge-Triggered Flip-Flops

 - The timing diagram for a D-type flip-flop is as follows:




- Note transitions on the output only occur at the (rising) clock edge

Edge-Triggered Flip-Flops

- **Latches** can be level-sensitive, i.e., their outputs change when the control (enable) input is high
- A **flip-flop** is a circuit that changes its outputs only at the **control signal's edges**
 - **Positive edge-triggered**: output changes when control goes from 0 to 1
 - **Negative edge-triggered**: output changes when control goes from 1 to 0
- We can build such circuits using a master-slave setup




Edge-Triggered Flip-Flops

- A few notes:
 - In this course, *latch* means **level-sensitive**, *flip-flop* means **edge-triggered** – correct modern convention
 - Flip-flops can be **positive edge-triggered** or **negative edge-triggered**
 - In our lectures, we will assume that flip-flops are positive edge-triggered unless we specify otherwise
 - Some older references may not follow this convention, so **be careful** when using other resources
 - Good news: the symbol for an edge triggered component always has a small triangle on the control input:

 

Edge-Triggered Flip-Flops

   - We've seen the D flip-flop:
 - Q takes the value on D at the rising edge of C
- There's also a J-K flip-flop:
 - Q becomes 1 if J is asserted at the rising edge and 0 if K is asserted
 - If both J and K are asserted, the output toggles at the rising edge
- And a T flip-flop:
 - Q toggles at the rising edge if T=1
- (Also a lesser seen SR flip-flop)




The Clock

- In synchronous design, we generally use one clock for all the sequential components in our circuit
- Hence, the outputs of all those blocks will only update at the clock (rising) edge
- That's why prefer (edge-triggered) flip-flops
- That way, we can more easily analyze our circuit, and model its behavior


Registers

 - The D-type flip-flop is the fundamental building block in synchronous design
- But we often deal with multi-bit signals
- When we combine multiple D flip-flops together to store multiple bits, we call this a **register**:




Registers

 - Henceforth, we can use only registers as our fundamental sequential component
- We now know how they are constructed internally, but we no longer need to worry about latches and flip-flops
- Even a 1-bit signal is stored in a “register”
- We can use a similar symbol to that used for a D flip-flop:



Registers

 - When dealing with multi-bit registers, we can show these values in a timing diagram without splitting up the bits:



- We can use decimal or hex, but make it clear
- Again, transitions only happen at the rising edge

Registers

- What about this arrangement?

