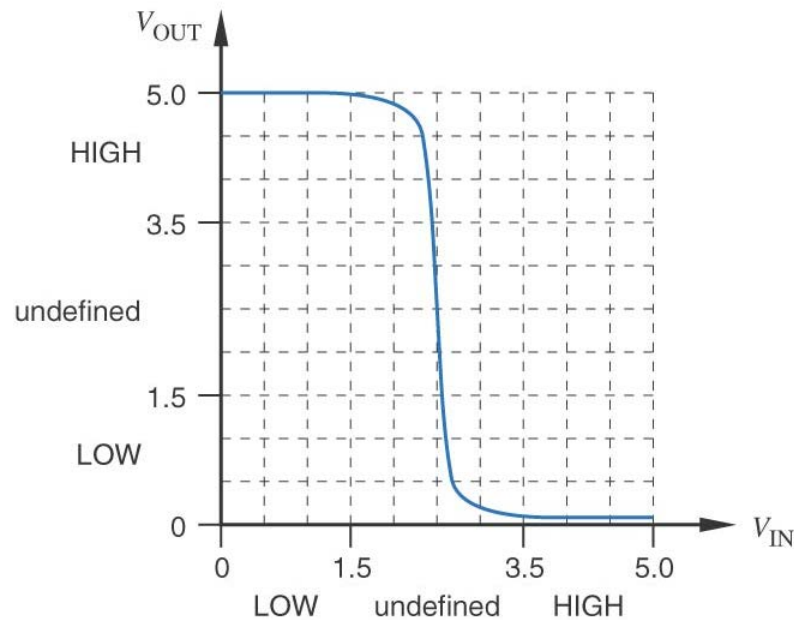


Digital Circuits Characteristics




Not
guaranteed


Fig. 3-25 Typical input-output transfer characteristic of a CMOS inverter

Schmitt-Trigger Inputs

Fig. 3-47


- A Schmitt-Trigger inverter is characterised by 2 threshold voltages: V_{T-} and V_{T+}
- When input voltage V_{IN} rises above V_{T+} , output V_{OUT} will switch to low.
- When input voltage V_{IN} drops below V_{T-} , output V_{OUT} will switch to high.
- This non-symmetric behaviour is called **hysteresis**.
- The symbol  indicates Schmitt-Trigger input.

Schmitt-Trigger Inverter

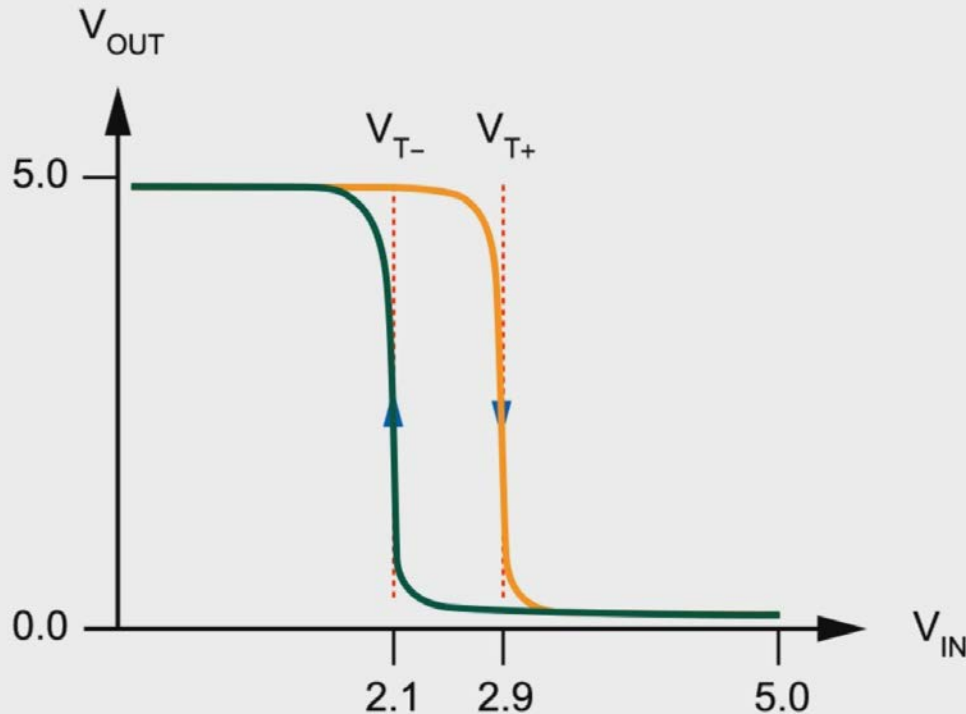

(a) input-output transfer characteristic

(b)

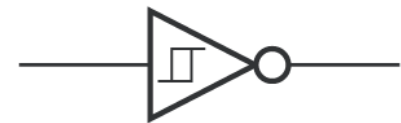

(b) logic symbol

Fig. 3-47 Schmitt-trigger inverter

Schmitt-Trigger Inverter

- Fig. 3-48
- When input voltage (V_{IN}) rises slowly, or has minor fluctuations around V_T , a standard inverter will give unstable, fluctuating output.
- The output of a Schmitt-Trigger inverter in such situations has clean transitions and does not fluctuate.

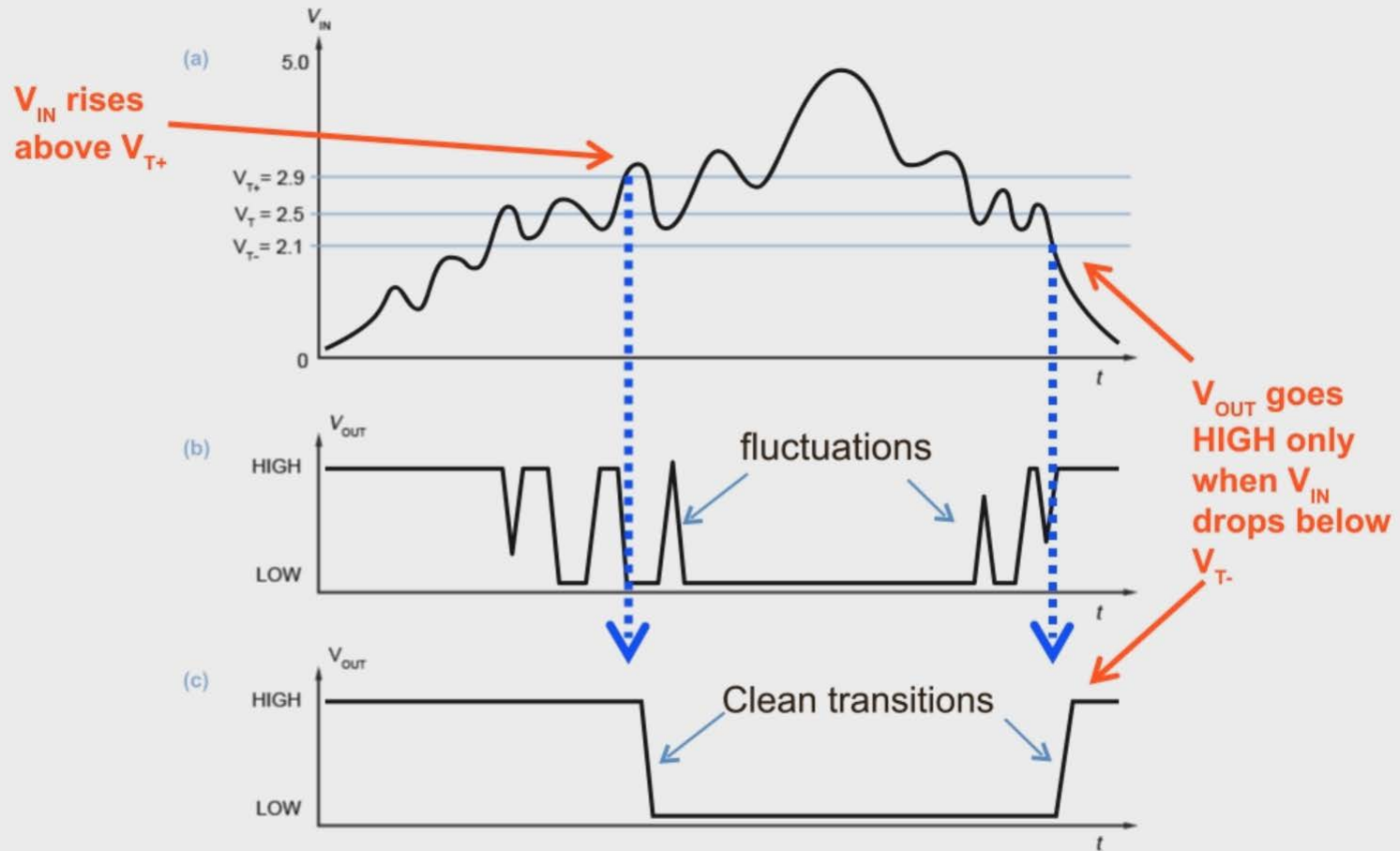


Fig. 3-48 Device operation with slowly changing inputs: (a) a noisy, slowly changing input; (b) output produced by an ordinary inverter; (c) output produced by an inverter with 0.8V of hysteresis.

Combinational PLA

- **PLD = Programmable Logic Devices**
- **Examples are PLA, PAL, CPLD, FPGA**
- **PLA: Programmable Logic Array**
- **PAL: Programmable Array Logic**
- **CPLD: Complex PLD**
- **FPGA: Field Programmable Gate Array**
- **SOM/SOP Boolean expressions can be easily implemented on a PLA**

PLA Example

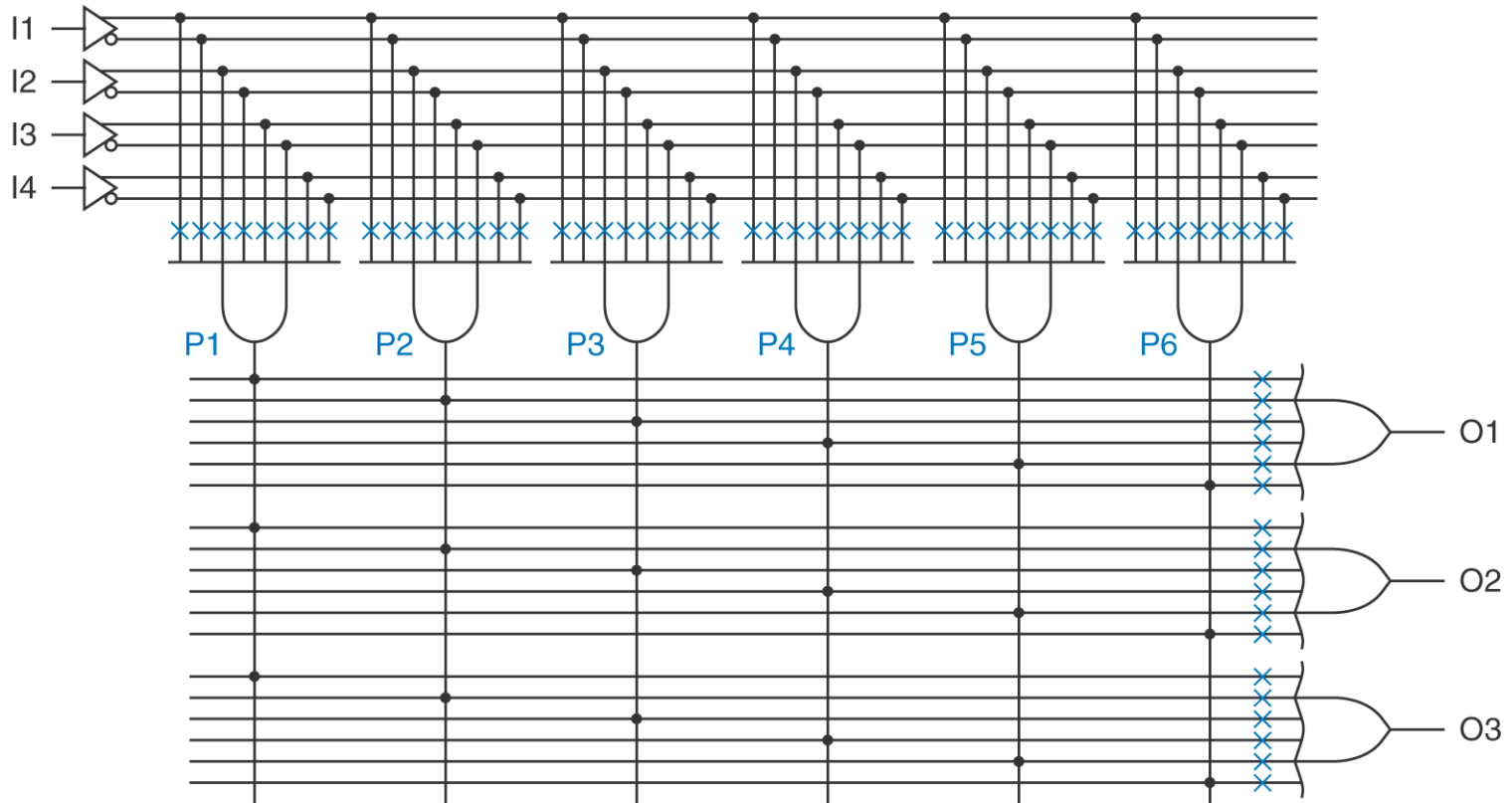


Figure 6-21

A 4×3 PLA with six product terms.

X : indicate programmable connections

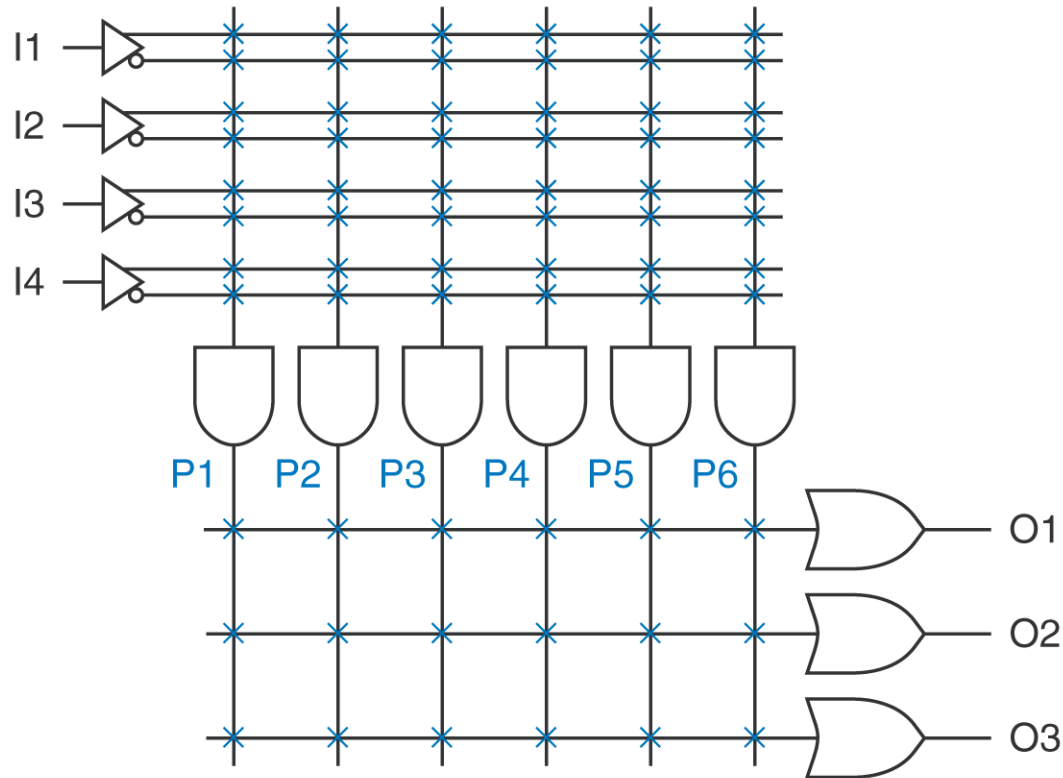


Figure 6-22

Compact representation of a 4×3 PLA with six product terms.

PLA Example: SOP implementation

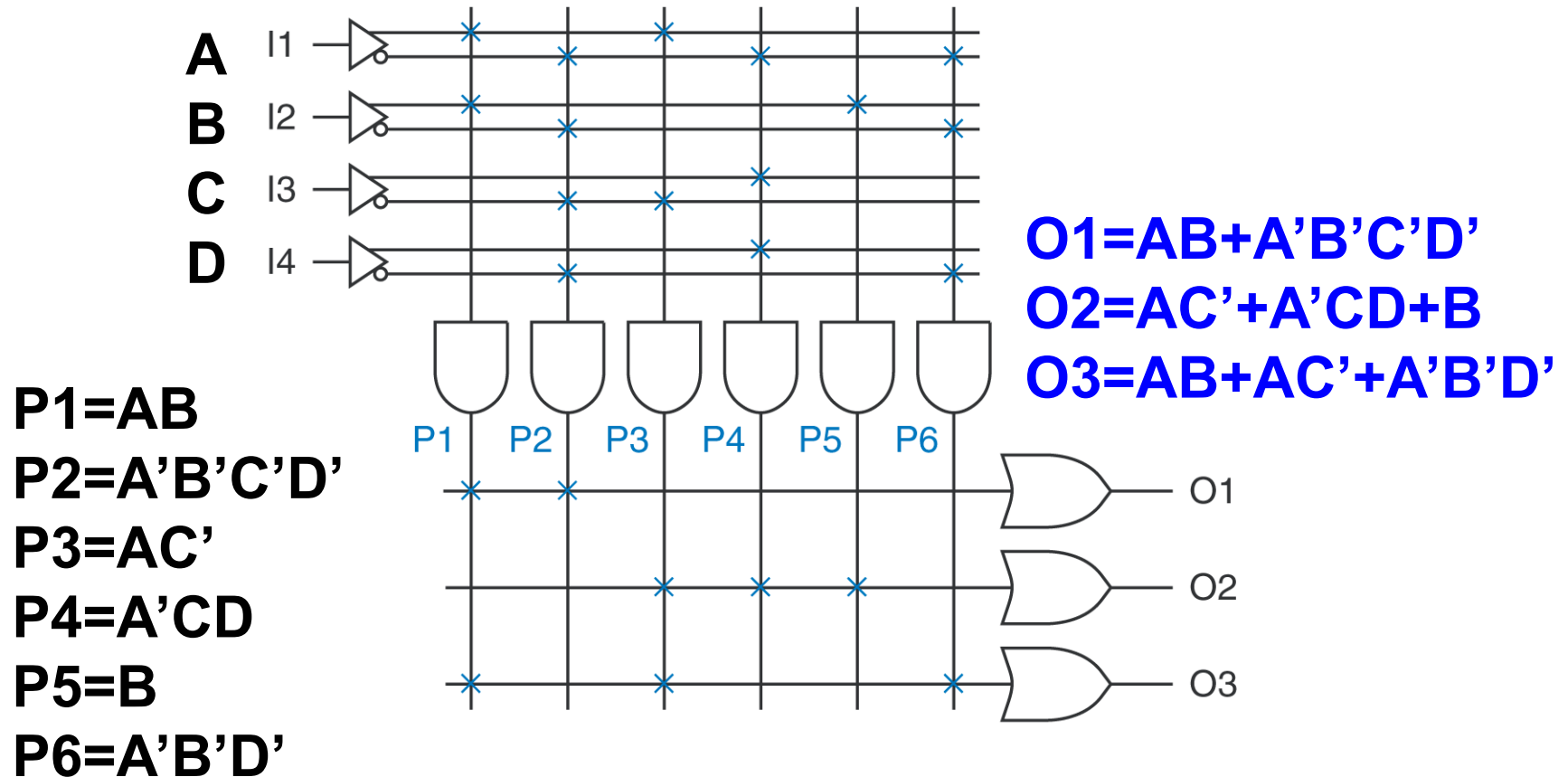


Figure 6-23

A 4×3 PLA programmed with a set of three logic equations.

PLA Example (truth table)


A	B	C	D	O1	O2	O3
0	0	0	0	1	0	1
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	1	0
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	0	1	1
1	0	0	1	0	1	1
1	0	1	0	0	1	0
1	0	1	1	0	1	0
1	1	0	0	1	1	1
1	1	0	1	1	1	1
1	1	1	0	1	1	1
1	1	1	1	1	1	1

Fixed-point numbers

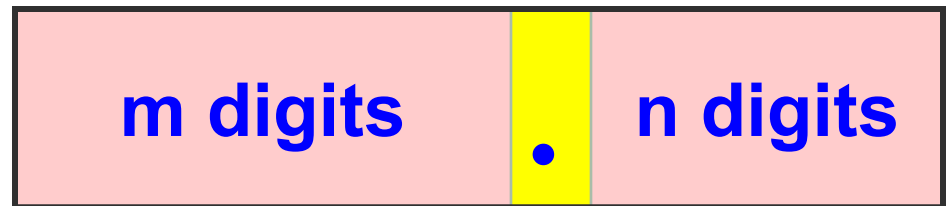Examples:

- 102_{10}
- 123.456_{10}
- $2000.AD_{16}$
- 1001.0101_2

The radix point
has a fixed
position among
the integer and
fraction digits



- **Fixed-point numbers are usually used for representing integers only**
- **Disadvantages of using fixed-point arithmetic for non-integers:**
 - **relatively small range of numbers that can be represented**
 - **possible loss of significant digits during computation**

Floating-point numbers

Machine equivalent of scientific notation

A floating-point number Z is represented as:

$$S \times R^E$$

e.g. 2.99792458×10^5

$$S \times R^E$$

Where


- S is the *significand*, usually a signed fractional fixed-point number
- R is the *radix* (e.g. 2 for binary, 8 for octal, 10 for decimal, etc.)
- E is the *exponent*, usually a signed fixed-point integer

Example: the IEEE Standard 754 on floating-point arithmetic

Single precision (32 bits):



Double precision (64 bits):

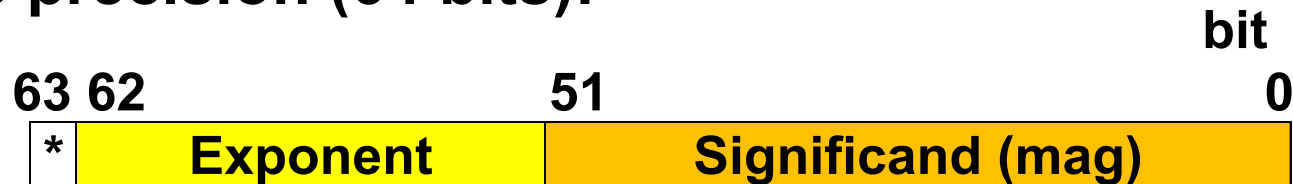

- * is the sign bit of significand
- radix is 2
- significand is in sign-magnitude notation
- exponent is in 2's complement notation