

21st CSEC – Past Year Paper Solution (2019 – 2020 Semester 1)

CE/CZ 1005 Digital Logic

1 (a) (i)

16	1835	
16	114	11 → B
	7	2

Ans. $1835_{10} = 72B_{16}$

(ii) Each digit in ASCII code is 7 bits so 8 digits are 56 bits.

Each digit in BCD is 4 bits so 8 digits are 32 bits.

(iii) $ACE6_{16} = (\underline{1}010\ 1100\ 1101\ 0110)_2$

Receiver checks parity – odd and concludes no error. Therefore, transmitter and receiver agree on odd parity.

(iv) 2's complement number: 10010111

Taking 1's complement, we get 01101000

Adding 1, we get 01101001

$$(01101001)_2 = 1 + 8 + 32 + 64 = 105_{10}$$

Signed decimal value = -105

Alternate method:-

Since 10010111 is a 2's complement number, the most significant bit (bold and underlined) determines the negative sign of the number, the decimal conversion can be carried out directly as –

$$(10010111)_2 = (-1) \times 2^7 + 2^4 + 2^2 + 2^1 + 2^0 = -128 + 16 + 4 + 2 + 1 = -105$$

(b)

$$\begin{aligned}
 F &= (w' + x + y + z') (w'y + xz')' (w'y' + xz)' \\
 &= (w' + x + y + z') (w'y)' (z')' (w'y')' (xz)' \quad [\text{De Morgan's law}] \\
 &= (w' + x + y + z') (w + y') (z) (w + y) (x' + z') \quad [\text{De Morgan's law and Involution law}] \\
 &= (w) (z) (x' + z') (x + y + w' + z') \quad [\text{Distributive law}] \\
 &= (wzx') (x + y + w' + z') \quad [\text{Distributive law}] \\
 &= (wzx'y) \quad [\text{Distributive law}]
 \end{aligned}$$

(c)

$$\begin{aligned}
 G(a, b, c, d) &= (a \text{ XOR } b) \text{ AND } (c \text{ XNOR } d) \\
 &= (a \oplus b) \cdot (c \odot d) \\
 &= (ab' + a'b) (cd + c'd')
 \end{aligned}$$

ab \ cd	00	01	11	10
00	0	0	0	0
01	1	0	1	0
11	0	0	0	0
10	1	0	1	0


Sum of minterms = $a'bc'd' + a'bcd + ab'c'd' + ab'cd$

ab \ cd	00	01	11	10
00	0	0	0	0
01	1	0	1	0
11	0	0	0	0
10	1	0	1	0

Product of maxterms = $(a+b)(c+d')(c'+d)(a'+b')$

(d)

$$W = (a+c) (b+d)' (e'f)'$$

 

W is low when –

i) Both a and c are low

OR

ii)

b	d
0	1
1	0
1	1

OR

ii) e is low and f is high

2

(a)

$$F = AB + (C^*)' (D^*) + (C^*)' (D^*) + A (C^*) (B)' (D^*)'$$

AB \ C*D*	00	01	11	10
00	0	1	0	0
01	0	1	0	0
11	1	1	1	1
10	0	1	0	1

Minimum cost SOP expression for $F = AC^*D + AB + CD^*$

$$G^* = AD^* + (A'BC^*D^*)$$

AB \ C*D*	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	0	1	1	0
10	0	1	1	0

Minimum cost POS expression for $G^* = (A+C^*)(A+B)(D^*)$

- (b) (i) Propagation delay is the average transition delay time for signal to propagate from input to output.
- (ii) Carry propagation is the propagation of the carry's addition. When two numbers are summed, if they overflow their place, we carry a one to the next place.
- (iii) Carry propagation can be reduced (hence increasing the speed of addition) by a special- purposed logic circuit called carry look-ahead circuit. A carry look-ahead adder improves speed by reducing the amount of time required to determine carry bits

- (c) (i) Device X
 High state DC noise margin = $V_{OH} - V_{IH} = 4.2 - 3.5 = 0.7$ volts
 Low state DC noise margin = $V_{IL} - V_{OL} = 1.5 - 0.7 = 0.8$ volts
 Fan-out = $\min([I_{OL} / I_{IL}], [I_{OH} / I_{IH}])$
 $= \min(18, 15)$
 $= 15$


Device Y
 High state DC noise margin = $4.5 - 3.6 = 0.9$ volts
 Low state DC noise margin = $1.8 - 0.5 = 1.3$ volts
 Fan-out = $\min([I_{OL} / I_{IL}], [I_{OH} / I_{IH}])$

$$= \min(13, 15) = 13$$

- (ii) Yes device X will be able to drive device Y. Fan-out of device X is 15. Fan-out of device Y is 13. Fan-out specifies the number of standard loads that the output gate can drive. Since fan-out of X is greater than fan-out of Y, device X can drive device Y.

- 3 (a) $x = 7'b1101101$
 $x = 7'b0011011$
 $x = 7'b1101111$
 $x = 7'b0000001$


(b)

 

 - (c) Lets assume from the perspective of each ant, a movement to the Left is a '0' and the Right is a '1'. Then, for NO collision, they must all go Left or all go Right. So, we need to detect 000 or 111 = no_col = 0.


```
module col_detect (input d1, d2, d3, output col);
    assign col = ({d1,d2,d3} == 3'b000) ? 0 : ({d1,d2,d3} == 3'b111) ? 0:1;
endmodule
```

- 4 (a) SR latch is the most basic circuit used for storing a bit.



An SR has two stable states, i.e., 0 and 1. The Q and not-Q outputs are supposed to be in opposite states. making both the S and R inputs equal to 1 result in both Q and not-Q being 0. For this reason, having both S and R equal to 1 is called an invalid or illegal state for the SR latch.

(b)

 

(c) (i) It is a Mealy FSM because the output can change in mid-state.

(ii) **module** FSM (Input RESET, CLK, T, output reg Y);
 parameter sta = 2'b00, stb = 2'b01, stc = 2'b10, std = 2'b11;
 reg [1:0] n, s;
 always @* begin
 if (RESET)
 s<=sta;
 else begin
 n = s; Y = 1'b0;
 case (s)
 sta: if(T) n = stb;
 stb: if(T) n = stc; else n = sta;
 stc: begin
 if(T) n = std;
 else n = stc;
 end
 std: if(!T) n = stc;
 endcase
 end
 end
endmodule