

# **CX1005**

## **Digital Logic**

### Verilog for Combinational Circuits

## So, Where are We?


- We have covered: **modules, ports, wires, module instantiation, gates** and **assign statements**

```
module myModule (input a, b, data_i,  
                 output flag, data_o, addr);  
  
    wire or1out;  
  
    get_Data IC1 (.din(data_i), .add(addr), .do(data_o));  
    or g1 (or1out, a, b);  
    assign flag = or1out & data_i;  
  
endmodule
```

- So far we have only examined **Structural Verilog**.
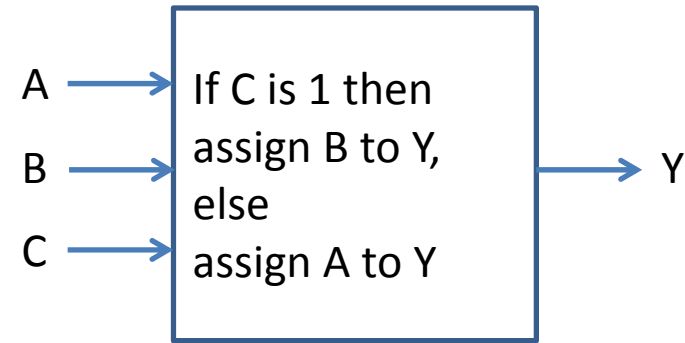
# Behavioral Modeling

- A more powerful level: we describe **how** the circuit **behaves**, not how it is *constructed*
- Synthesis tools work out how to make hardware that fulfills the description, taking into account the target architecture



```
module counter (clk,  
reset, enable, count);  
  input clk, reset,  
  enable;  
  output [3:0] count;  
  reg [3:0] count;  
  
  always @ (posedge clk)  
  if (reset == 1'b1)  
    count <= 0;  
  else if (enable == 1'b1)  
    count <= count + 1;  
  
endmodule
```



Tools  
(e.g. Logic  
Synthesizer)



## Combinational always Block

- For *behavioral design*, we use a type of procedural block called an **always** block
- An **always** block contains procedural statements that describe the behavior of the desired hardware

```
always @ (a, b)
begin
    x = a & b;
    y = a | b;
end
```

Sensitivity List

Procedural statements

- The **always** keyword starts a block
- The *sensitivity list* **must** contain the names of any signals that affect the output of the block

## always @ \*

- If you accidentally leave a signal out you will not get the expected circuit
- Luckily, there's a shortcut: **always @ \*** – use it!

```
always @ (a, b)
begin
    x = a & b;
    y = a | b;
    z = a & c;
end
```

This will not generate the expected output as it will not be triggered when input c changes

```
always @ *
begin
    x = a & b;
    y = a | b;
    z = a & c;
end
```

The “\*” means all input signals inside the block.

This is OK. Whenever any signal changes (\* means all input signals) a change in the output is forced.

## Combinational always Block

- The statements can be assignments as in the example or more complex structures
- You do not use the **assign** keyword inside an always block, **ever ....**
- If there is more than one statement, use **begin** and **end** to define the start and end of the block.

```
always @ *  
begin  
    x = a & b;  
    y = a | b;  
    z = a & c;  
end
```

## Reg

- Signals you assign to from within an ***always** block*
  - Must be declared as being of type: **reg**
- **reg** is synonymous with wire, but these signals can be assigned to from inside an always block, **wires** cannot!
- A **wire** is simply a *connection*, it holds no value of its own
- The **reg** type is more like a *variable* in programming, as we will see
- Note: you *cannot* assign to a **reg** signal using an ***assign** statement*, or connect it to module instance outputs.

```
module temp (input a, b,  
             output out);  
  
    wire w1;  
  
    assign w1 = a & b;  
    assign out = w1;  
  
endmodule
```

```
module temp (input a, b,  
             output out);  
  
    reg w1;  
  
    always @ *  
        w1 = a & b;  
  
    assign out = w1;  
endmodule
```

## Reg

- Declare **reg** signals:
  - You can set an *initial value* when you declare **reg** signals

```
reg a, b;  
reg [3:0] x = 4'b0000;
```

- You can also declare your module outputs as **reg** if you plan to assign to them directly from within an **always** block:

```
module sel_one (input [5:0] a, b, c, d,  
               input [1:0] sel,  
               output reg [5:0] sigsel);
```



## So What is Synthesized?

- Assignments in an **always** block are exactly the same as assignments using an **assign**:

```
always @ *  
begin  
    x = a & b;  
    y = a | b;  
end
```



```
assign x = a & b;  
assign y = a | b;
```

**Exactly the same circuit will be synthesized**

## If Statement

- With always blocks, we can use some powerful constructs:
- **If** statement:

```
always @ *  
begin  
    if (x < 6)  
        alarm = 1'b0;  
    else  
        alarm = 1'b1;  
end
```

- You can have more than one statement in each branch. If so, you use **begin** and **end**

```
always @ *  
begin  
    if (alarm == 1'b1)  
        begin  
            if (after_hours)  
                siren = 1'b0;  
            else  
                siren = 1'b1;  
                light = 1'b1;  
            end  
        else  
            begin  
                siren = 1'b0;  
                light = 1'b0;  
            end  
        end  
end
```

## A note on begin and end

- Verilog follows C standards for blocks
- The difference is that Verilog uses **begin** and **end**, rather than { }
  - **Note { } is used for concatenation**
- If there is just one statement in the body of a statement (like if, for, or always block), then there is no need for **begin** and **end**
- If there is more than 1 statement, you must use **begin** and **end**

```
always @ *  
begin  
  
if (x < 6)  
    alarm = 1'b0;  
else  
    alarm = 1'b1;  
  
end
```

```
always @ *  
if (x < 6)  
begin  
    alarm = 1'b0;  
end  
else  
begin  
    alarm = 1'b1;  
end  
end
```

**These are the same**

```
always @ *  
if (x < 6)  
    alarm = 1'b0;  
else  
    alarm = 1'b1;
```



# Case Statement

- We can use **case** statements:

```
always @ *  
case (sel)  
    2'b00    : y = a;  
    2'b01    : y = b;  
    2'b10    : y = c;  
    default  : y = 4'b1010;  
endcase
```

```
always @ *  
case (sel)  
    2'd0      : y = a;  
    2'd1      : begin  
                    y = b;  
                    z = c;  
                end  
    2'd2      : y = c;  
    default   : y = 4'b1010;  
endcase
```

- There is no need for a break in each branch (unlike some software languages)

# Implementing Decoder with Verilog


Input      Output

00 → 0001

01 → 0010

10 → 0100

11 → 1000

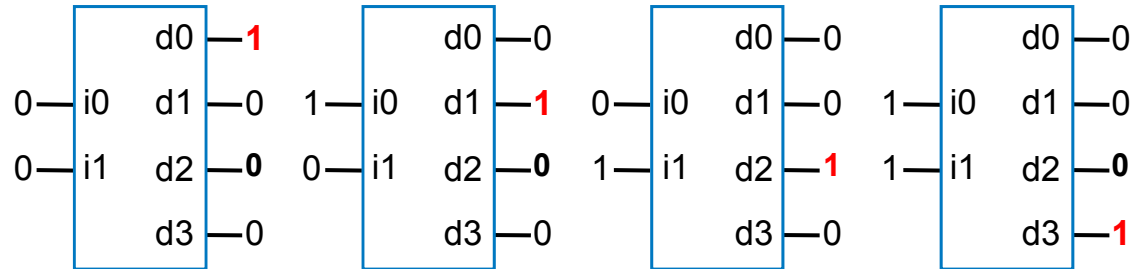

- Example: 3-to-8 decoder:

Input      Output

000 → 00000001

001 → 00000010

010 → 00000100

011 → 00001000

...

111 → 10000000

```
module decoder3_8(output reg [7:0] d_out,
                  input  [2:0] ival);
```

```
always @ *
```

```
case(ival)
```

```
3'b000 : d_out = 8'b00000001;
```

```
3'b001 : d_out = 8'b00000010;
```

```
3'b010 : d_out = 8'b00000100;
```

```
3'b011 : d_out = 8'b00001000;
```

```
3'b100 : d_out = 8'b00010000;
```

```
3'b101 : d_out = 8'b00100000;
```

```
3'b110 : d_out = 8'b01000000;
```


```
3'b111 : d_out = 8'b10000000;
```

```
endcase
```

```
endmodule
```

# Implementing Multiplexer with Verilog


1-bit 4x1 mux

 

```
module mux4 (output reg q,  
             input [3:0] d,  
             input [1:0] sel);  
  
    always @ * begin  
        case (sel)  
            2'b00 : q = d[0];  
            2'b01 : q = d[1];  
            2'b10 : q = d[2];  
            2'b11 : q = d[3];  
        endcase  
    end  
endmodule
```

Note the begin and end.  
These are not needed as a  
case is a single statement.  
But makes it easier to read!!

# Implementing Multiplexer with Verilog

 

```
module mux_4_32(output [7:0] mxout,  
               input  [7:0] in3, in2,  
               input  [7:0] in1, in0,  
               input  [1:0] sel,  
               input          enable);  
  
    reg [7:0] mux_int;  
    assign mxout = enable ? mux_int : 8'd0;  
    always @ *  
    begin  
        case(sel)  
            2'b00    : mux_int = in0;  
            2'b01    : mux_int = in1;  
            2'b10    : mux_int = in2;  
            2'b11    : mux_int = in3;  
        endcase  
    end  
endmodule
```







# **IMPORTANT CONSIDERATIONS IN BEHAVIORAL VERILOG**

## Signal Assignments - always Block

- Notice that we can assign to *multiple* signals from inside one **always** block
- If you assign to a signal from inside an **always** block, you must **never** assign to it from **anywhere else!**
- That is, not from:
  - **assign** statements
  - Other **always** blocks
- Each **always** block represents the logic that generates a certain signal or set of signals
  - Hence, you should only assign to those signal(s) from inside that **always** block
- Only group signals into a single **always** block if it makes sense to do so – generally when they follow similar logic

```
assign x = . . .; 
```


```
always @ *  
begin  
    x = a & b;  
    y = a | b;  
end
```

```
always @ *  
begin  
    y = . . .;  
end 
```

## Statement Order in always block


- The issue of statement order can be a little confusing
- When we read the statements in an **always** block, we read them in order, and **order matters**
- The synthesis tools turn the combined behavior described into a piece of combinational hardware
- Hence, if we assign to a signal more than once, in the end, the last assignment wins, since that's what the tools will use

```
always @ *  
begin  
    x = a & b;  
    y = x | c;  
    y = x ^ c;  
end
```

 
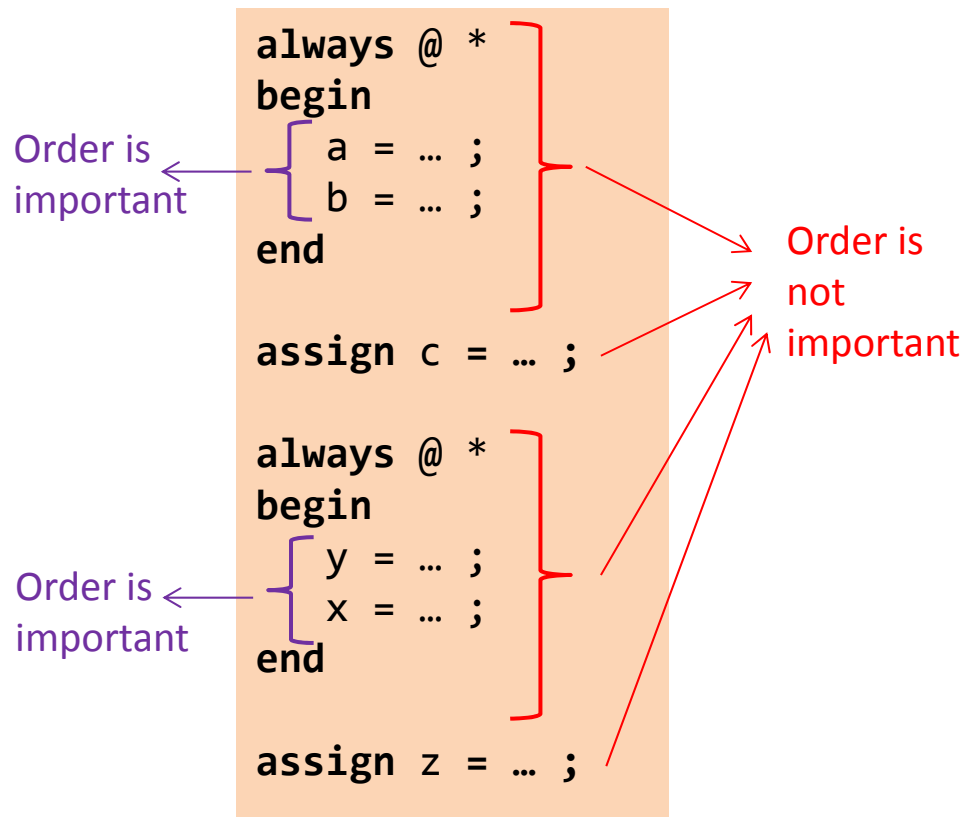
## Multiple always blocks

- The order of multiple **always** blocks in a module doesn't matter
  - They occur concurrently
- You can have as many **always** blocks as you want, and they each implement a piece of concurrent hardware



```
assign z = ... ;  
assign c = ... ;  
  
always @ *  
begin  
  y = ... ;  
  x = ... ;  
end  
  
always @ *  
begin  
  a = ... ;  
  b = ... ;  
end
```

## Avoiding Latches

- What happens to *y* in the **else** branch?

```
always @*  
begin  
    if(valid) begin  
        x = a | b;  
        y = c;  
    end  
    else  
        x = a;           //y?  
end
```



- This would imply *y* should keep its value – This is the behavior of a latch not combinational logic!

## Avoiding Latches

- One way to fix this is to use a default assignment at the top of the **always** block:



```
always @*  
begin  
    y = x;  
    if(valid) begin  
        c = a | b;  
        y = z;  
    end  
    else  
        c = a;  
end
```

- The default is overwritten by any subsequent assignment
- Assignments at the top of an **always** block are hence a great way of remembering to assign to all your signals

## Avoiding Latches

```
always @ *  
  case (sel)  
    2'b00 : y = a;  
    2'b01 : begin  
              y = b;  
              z = c;  
            end  
    2'b10 : y = c;  
    default : y = 4'b1010;  
  endcase
```



```
always @ *  
begin  
  z = a;           // default  
  y = 4'b1010;    // default  
  case (sel)  
    2'b00 : y = a;  
    2'b01 : begin  
              y = b;  
              z = c;  
            end  
    2'b10 : y = c;  
  endcase  
end
```

But, as we only assign to z in one instance, this implies that you are storing the data. **Must not do this as it synthesises storage.**



## Summary

- You must always include *any* signal that affects the output in the *sensitivity list*
  - else the synthesizer will produce something unexpected!!
  - So, easier to just use **always @ \***
- You must assign to the output signal in **all** possible cases
  - As you are designing combinational logic, it makes no sense to sometimes assign and other times not – that implies storing a value – That is not combinational logic
  - If you forget to do this, you will end up with a latch in your circuit, which is not wanted!!!
  - More on this when you start to look at **Sequential Circuits**

