

5. Combinational Logic Circuits

- The most common type of digital logic circuits
- Made up of combinations of logic gates
- At any point in time, the output logic level only depends on the present combination of logic levels at the N inputs
 - $O(t) = f [I_1(t), I_2(t), I_3(t), \dots, I_N(t)]$
- It has no memory characteristics, unlike sequential circuits
- Relatively easy to analyse and design compared to sequential circuits

Designing and Implementing a Combinational Logic Circuit

- **The function of a required logic circuit can be fully described by a truth table**
- **To design the circuit, we obtain the Boolean expression from the truth table**
- **The Boolean expression can then be implemented using a proper choice of logic gates**

A Boolean expression is also known as

- **a Boolean equation**
- **a logic function**

**It fully describes, algebraically,
the logic circuit's output in response
to every possible input condition.**

**For simple circuits, the expression can
usually be obtained by observation.**

Forms of Boolean Expressions

- **Canonical Form**
 - Sum of minterms expression (SOM)
 - Product of maxterms expression (POM)
- **Standard Form**
 - Sum of products expression (SOP)
 - Product of sums expression (POS)

- **minterms:**

- All possible combinations of a given set of Boolean variables formed by the **AND** operation

- **maxterms:**

- All possible combinations of a given set of Boolean variables formed by the **OR** operation

A logic circuit with 2 inputs X and Y will have these 4 minterms and maxterms:

inputs		minterms		maxterms	
X	Y				
0	0	$X' \cdot Y'$	m0	$X + Y$	M0
0	1	$X' \cdot Y$	m1	$X + Y'$	M1
1	0	$X \cdot Y'$	m2	$X' + Y$	M2
1	1	$X \cdot Y$	m3	$X' + Y'$	M3

A minterm or maxterm uniquely describes the input combination at a given time instant

A logic circuit with 3 inputs X, Y and Z will have these 8 minterms and maxterms:

inputs			minterms		maxterms	
X	Y	Z				
0	0	0	$X' \cdot Y' \cdot Z'$	m0	$X + Y + Z$	M0
0	0	1	$X' \cdot Y' \cdot Z$	m1	$X + Y + Z'$	M1
0	1	0	$X' \cdot Y \cdot Z'$	m2	$X + Y' + Z$	M2
0	1	1	$X' \cdot Y \cdot Z$	m3	$X + Y' + Z'$	M3
1	0	0	$X \cdot Y' \cdot Z'$	m4	$X' + Y + Z$	M4
1	0	1	$X \cdot Y' \cdot Z$	m5	$X' + Y + Z'$	M5
1	1	0	$X \cdot Y \cdot Z'$	m6	$X' + Y' + Z$	M6
1	1	1	$X \cdot Y \cdot Z$	m7	$X' + Y' + Z'$	M7

For N-inputs, there will be 2^N minterms

e.g. 4 inputs: a, b, c, d

- 13 in decimal = 1101 in binary
- Then **minterm m13** = a b c' d
- **maxterm M13** = a' + b' + c + d'
- 2 in decimal = 0010 in binary
- Then **minterm m2** = a' b' c d'
- **maxterm M2** = a + b + c' + d

- **Minterms** are formed such that given a set of input conditions, only the corresponding minterm (but not the other minterms) will **yield a logic 1**.
- Eg. $x=0, y=1, z=1$ the corresponding minterm is m_3 , i.e. $x'yz$
- Substituting the values of x, y and z will result in $m_3 = x'yz = 0' \cdot 1 \cdot 1 = 1$
- Notice that by arranging x, y, z together to form a 3-bit binary number (MSB= x , LSB= z), the decimal equivalent is used to denote the minterm number ($011_2 = 3_{10}$ in this example)

- **Maxterms** are formed such that given a set of input conditions, only the corresponding maxterm (but not the other maxterms) will **yield a logic 0**.
- eg. $x=1, y=0, z=1$ the corresponding maxterm is M_5 , i.e. $x' + y + z'$
- Substituting the values of x, y and z will result in $M_5 = x' + y + z' = 1' + 0 + 1' = 0$
- Notice that arranging x, y, z together to form a 3-bit binary number (MSB= x , LSB= z), the decimal equivalent is used to denote the maxterm number ($101_2 = 5_{10}$ in this example)

The Sum of minterms expression

To write the sum-of-minterms

Boolean expression from a truth table:

- **For each combination of the input variables that produces a logic 1 in the output, collect the corresponding minterms and **OR** them together**

The Product of maxterms Expression

- For each combination of the input variables that produces a logic 0 in the output, collect the corresponding maxterms and **AND** them together
- Conversion between the two forms is easy.
- Sum of minterms expression is associated with **active HIGH** output.
- Product of maxterms expression is associated with **active LOW** output.

Example: given the truth table, obtain the SOM and POM expressions for output F

inputs			Output F
X	Y	Z	
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

inputs			minterms		maxterms		F
X	Y	Z					
0	0	0	$X' \cdot Y' \cdot Z'$	m0	$X + Y + Z$	M0	0
0	0	1	$X' \cdot Y' \cdot Z$	m1	$X + Y + Z'$	M1	1
0	1	0	$X' \cdot Y \cdot Z'$	m2	$X + Y' + Z$	M2	1
0	1	1	$X' \cdot Y \cdot Z$	m3	$X + Y' + Z'$	M3	0
1	0	0	$X \cdot Y' \cdot Z'$	m4	$X' + Y + Z$	M4	1
1	0	1	$X \cdot Y' \cdot Z$	m5	$X' + Y + Z'$	M5	0
1	1	0	$X \cdot Y \cdot Z'$	m6	$X' + Y' + Z$	M6	0
1	1	1	$X \cdot Y \cdot Z$	m7	$X' + Y' + Z'$	M7	1

$$F = X'Y'Z + X'YZ' + XY'Z' + XYZ$$

$$= \Sigma_{XYZ} (1, 2, 4, 7)$$

SOM

$$F = (X+Y+Z) (X+Y'+Z') (X'+Y+Z') (X'+Y'+Z)$$

$$= \Pi_{XYZ} (0, 3, 5, 6)$$

POM

Other ways of writing canonical expressions:

$$F = \sum_{xyz} (1, 2, 4, 7)$$

SOM

$$F(X,Y,Z) = \sum m (1, 2, 4, 7)$$

$$F(X,Y,Z) = m1 + m2 + m4 + m7$$

$$F = \prod_{xyz} (0, 3, 5, 6)$$

POM

$$F(X,Y,Z) = \prod M (0, 3, 5, 6)$$

$$F(X,Y,Z) = M0 \cdot M3 \cdot M5 \cdot M6$$

Interpretation of **active High** and **active Low** for the above example:

Value of Output F	Interpretation of output F	
	There is an <u>odd</u> number of 1's among the 3 inputs X, Y, Z	There is an <u>even</u> number of 1's among the 3 inputs X, Y, Z
1 (High)	TRUE	FALSE
0 (Low)	FALSE	TRUE

- E.g. rename F as **ODD**, which is **active High** (usually write Som expression)
- E.g. rename F as **EVEN***, which is **active Low** (usually write PoM expression)

Standard Form of Boolean Expressions

- **SOP and POS**
- **Simplified expressions from the canonical forms**
- **Leads to simpler logic circuits**
- **Known as combinational circuit minimisation**
- **Minimise the number of gates (minimum number of product terms or sum terms)**
- **Minimise the number of inputs on each gate (minimum number of input variables in each product term and sum term)**

Sum of products (SOP) expression

example:

This is a sum-of-minterms expression:

$$f(x, y, z) = xyz' + xyz + x'y'z + xy'z$$


Simplifying, we get

$$\begin{aligned} f(x, y, z) &= xy(z' + z) + (x' + x)y'z \\ &= xy + y'z \end{aligned}$$

This is now a sum-of-products expression.

A **product term** need not contain all the input variables, unlike a **minterm**.

Product of sums (POS) expression

example:

This is a product-of-maxterms expression:

$$f(x, y, z) = (x+y'+z')(x+y'+z)(x'+y'+z)(x'+y+z)$$


Simplifying, we get

$$f(x, y, z) = (x + y')(x' + z)$$

This is now a product-of-sums expression.

A **sum term** need not contain all the input variables, unlike a **maxterm**.

These are **neither SOP nor POS** expressions:

$$f = (xy)'z + xz'$$

not a product term

$$f = xy(x' + z)'$$

not a sum term

$$f = (xy + z)(x' + y)$$

not a sum term

Use the standard form (i.e. SOP or POS) wherever possible.

Obtaining Simplified Standard Expressions from the Canonical Form

- **Different methods for Boolean expression simplification**
 - Algebraic method
 - Karnaugh map (K-map)
 - Quine-McCluskey method (Q-M method or tabulation method)
 - Heuristic methods, e.g. Espresso-II

Simplified Boolean expressions yield

- **Simpler circuits with fewer logic gates**
- **Fewer connections**
- **Lower cost**
- **Improved reliability**

Algebraic method

- **Use Boolean theorems**
- **Requires experience and skills**

**Examples:
simplify**

$$Z = ABC + AB'(A'C')'$$



$$Z = AB' + AC$$

simplify

$$X = (A' + B)(A + B + D)D'$$



$$X = BD'$$

Karnaugh Map

- Graphical method
- Easier to use than algebraic method
- Based on the Boolean theorems
$$AB + AB' = A(B + B') = A \text{ (for SOP)}$$
$$(A+B)(A+B') = A \text{ (for POS)}$$
- Truth table gives value of output X for each combination of input values. K-map gives the same info in a different format.

- K-map squares are labelled such that adjacent squares differ only in one variable.
- **SOP** expression for output X can be obtained by **OR**ing together those squares that contain a **1**.
- Can also obtain **POS** expression by **AND**ing together those squares that contain a **0**.
- Note the correspondence with **SOM** (think **1**) and **POM** (think **0**).

Truth Table to K-Map Conversion [2 Inputs]

$$X = A'B' + AB$$

A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

K-map

X	B=0	B=1
A=0	1	0
A=1	0	1

Truth Table to K-Map Conversion [3 Inputs]

$$X = A'B'C' + A'B'C + A'BC' + ABC'$$

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

K-map

X	C=0	C=1
A=0,B=0	1	1
A=0,B=1	1	0
A=1,B=1	1	0
A=1,B=0	0	0

Truth Table to K Map Conversion [4 Inputs]

A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

$$X = A'B'C'D + A'BC'D + ABC'D + ABCD$$


		C, D			
A, B	X	0 0	0 1	1 1	1 0
	0 0	0	1	0	0
	0 1	0	1	0	0
	1 1	0	1	1	0
	1 0	0	0	0	0

Truth Table to K Map Conversion [4 Inputs]


A	B	C	D	dec
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

		C, D			
		X			
		0 0	0 1	1 1	1 0
A, B	0 0	0	1	3	2
	0 1	4	5	7	6
	1 1	12	13	15	14
	1 0	8	9	11	10

Kmap: Looping 2 “neighbouring” 1’s

 

Kmap: Looping 4 “neighbouring” 1’s

 

Kmap: Looping 8 “neighbouring” 1’s

A, B

X	C, D			
	0 0	0 1	1 1	1 0
0 0	0	1	1	0
0 1	0	1	1	0
1 1	0	1	1	0
1 0	0	1	1	0

A red circle highlights the 8 '1's in the central 2x2 area of the K-map (the 2x2 subgrid where C and D are 01 or 11 and A and B are 00, 01, 11, or 10). A red arrow points from the top-right corner of this circle to a red **D**, indicating that the loop represents the variable D.

Note these rules on Kmap for simplification:

- Loop **1**'s to obtain **SOP** expression.
 - Only 2^N number of “neighbouring” 1's can be looped together.
 - No looping along diagonal.
 - All **1**'s must be looped.
 - Use the biggest loops and the fewest loops.
 - A square(s) may be looped more than once.
 - **Each loop of 1's will yield a product term.**
-
- **0**'s can also be looped in a similar manner to obtain **POS** expression.
 - **Each loop of 0's will yield a sum term.**

Example: Simplify the Boolean expression for output Z using K-map

A	B	C	D	Z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Example (cont)

Step 1 : Convert truth table to K-map

Step 2 : Loop adjacent 1's to get SOP

	CD			
Z	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	1	1	1	1
10	1	1	1	1

AB

BCD


A

$$Z = A + BCD$$

Example (cont)

Alternatively

Step 2 : Loop adjacent 0's to get POS

 

$$Z = (A + B)(A+C)(A+D)$$

Don't care conditions

- **Some logic circuits can be designed such that there are certain input conditions for which there are **no specified output levels**.**
- **This is possible because**
 - **These input conditions will not occur**
 - **It does not matter whether the output is 0 or 1**
- **The designer is free to make the output for any “don't care” condition to be 0 or 1 in order to produce the simplest output expression.**

Example: Design a logic circuit whose input is a BCD digit, and whose output goes HIGH if the input is smaller than 6_{10}

A	B	C	D	Z
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

X denotes “don’t care”

Example (cont):

Design 1: SOP

$$Z = A'B' + A'C'$$

		CD			
Z		00	01	11	10
00	1	1	1	1	1
01	1	1	0	0	0
11	X	X	X	X	X
10	0	0	X	X	X

AB

X denotes “don’t care”

Example (cont):

Design 2: SOP

$$Z = A'B' + BC'$$

		CD			
Z		00	01	11	10
00	1	1	1	1	1
01	1	1	0	0	0
11	X	X	X	X	X
10	0	0	X	X	X

AB

X denotes “don’t care”

Example (cont):

Design 3: SOP

$$Z = B'C + A'C'$$

	CD			
Z	00	01	11	10
00	1	1	1	1
01	1	1	0	0
11	X	X	X	X
10	0	0	X	X

AB

X denotes “don’t care”

Example (cont):

Design 4: POS

$$Z = (A' + B + C)(A + B' + C')$$

		CD			
Z		00	01	11	10
00		1	1	1	1
01		1	1	0	0
11		X	X	X	X
10		0	0	X	X

AB

X denotes “don’t care”

Example (cont):

Design 5: POS

$$Z = A' (B' + C')$$

	CD			
Z	00	01	11	10
00	1	1	1	1
01	1	1	0	0
11	X	X	X	X
10	0	0	X	X

AB

X denotes “don’t care”

Don't cares

- “Don't cares” can be looped in a similar way on the Karnaugh map.
- When looped with **1**'s to write **SOP** expression, the “don't care” is treated as **1**. Those “don't cares” not looped are treated as **0**.
- Conversely, when looped with **0**'s to write **POS** expression, the “don't care” is treated as **0**. Those “don't cares” not looped are treated as **1**.
- “Don't cares” should only be looped if it helps to simplify a Boolean expression (i.e. helps to form a bigger loop).

Summary: Designing a Combinational Logic Circuit

- 1 From problem specifications, derive the relationship between the output(s) and the inputs. This can be expressed in the form of a truth table.**
- 2 Obtain the Boolean expression that relates the desired output to the inputs. It can either be in SOP or POS form, although SOP is usually used.**
- 3 Simplify the expression using either algebraic, K-map or QM method.**
- 4 Implement the circuit from the simplified expression. Certain restrictions may need to be taken into account, eg. use only 2-input NAND gates.**

Enable/Disable Circuits

Enable

A logic circuit is said to be enabled if the **output is allowed to change** in response to changes in the inputs.

Disable/Inhibit

A logic circuit is said to be disabled/inhibited if the **output is not allowed to change** in response to changes in the inputs.

The output is either fixed at 0 (typically for active High output) or 1 (typically for active Low output).

 
 
 
 
 
 
 
 


Fig. 4-26 (Tocci 10th ed.)

Enable/Disable Example

Inputs		Output	Effect of output
Child Safe	Unlock	Open	
0	X	0	Door closed
1	0	0	Door closed
1	1	1	Door opened

X: “don’t care”, i.e. can be 0 or 1

- **Circuit is enabled when ChildSafe=1; the output Open changes with input Unlock.**
- **Circuit is disabled when ChildSafe=0; Open is stuck at 0.**