


CX1005

Digital Logic

Introduction to Verilog

Where is this going?

 - Designs are getting bigger and more complex
 - Designer productivity is an issue



So is working with individual gates going to allow you to design a 2 billion transistor CPU?

What about using Schematic Capture? Will that allow you to design a 2 billion transistor CPU?

So we need better Design Methods and Tools (EDA and CAD tools) to design large complex systems.

Verilog and the **FPGA tools** are starting you along this path...

Next, we will cover:

- Introduction to Verilog HDL
 - Verilog is a hardware description language (HDL) and has some similarities to programming languages
- Combinational circuits in Verilog
 - Combinational circuits are circuits where the current outputs depend only on the current inputs
 - So far you have only looked at gate level combinational circuits
- Sequential circuits
 - Sequential circuits are circuits where the outputs depend on both the present input signals and on the past history of the inputs. That is it contains memory.
 - We will only consider synchronous (clocked) circuits.
- State machines
 - A state machine is a sequential circuit with a finite number of states which can be used to control the operation of physical devices

Hardware Description Languages (HDLs)

- Special languages with special constructs for describing hardware
- They can be used to describe hardware
 - At various levels of abstraction
 - Enables hierarchical design
- Sophisticated tools can then ensure the hardware generated from the description is efficient

```
module counter (clk,  
reset, enable, count);  
  input clk, reset,  
  enable;  
  output [3:0] count;  
  reg [3:0] count;  
  
  always @ (posedge clk)  
  if (reset == 1'b1)  
    count <= 0;  
  else if (enable == 1'b1)  
    count <= count + 1;  
  
endmodule
```




Tools
(e.g. Logic
Synthesizer)



Hardware Description Languages (HDLs)

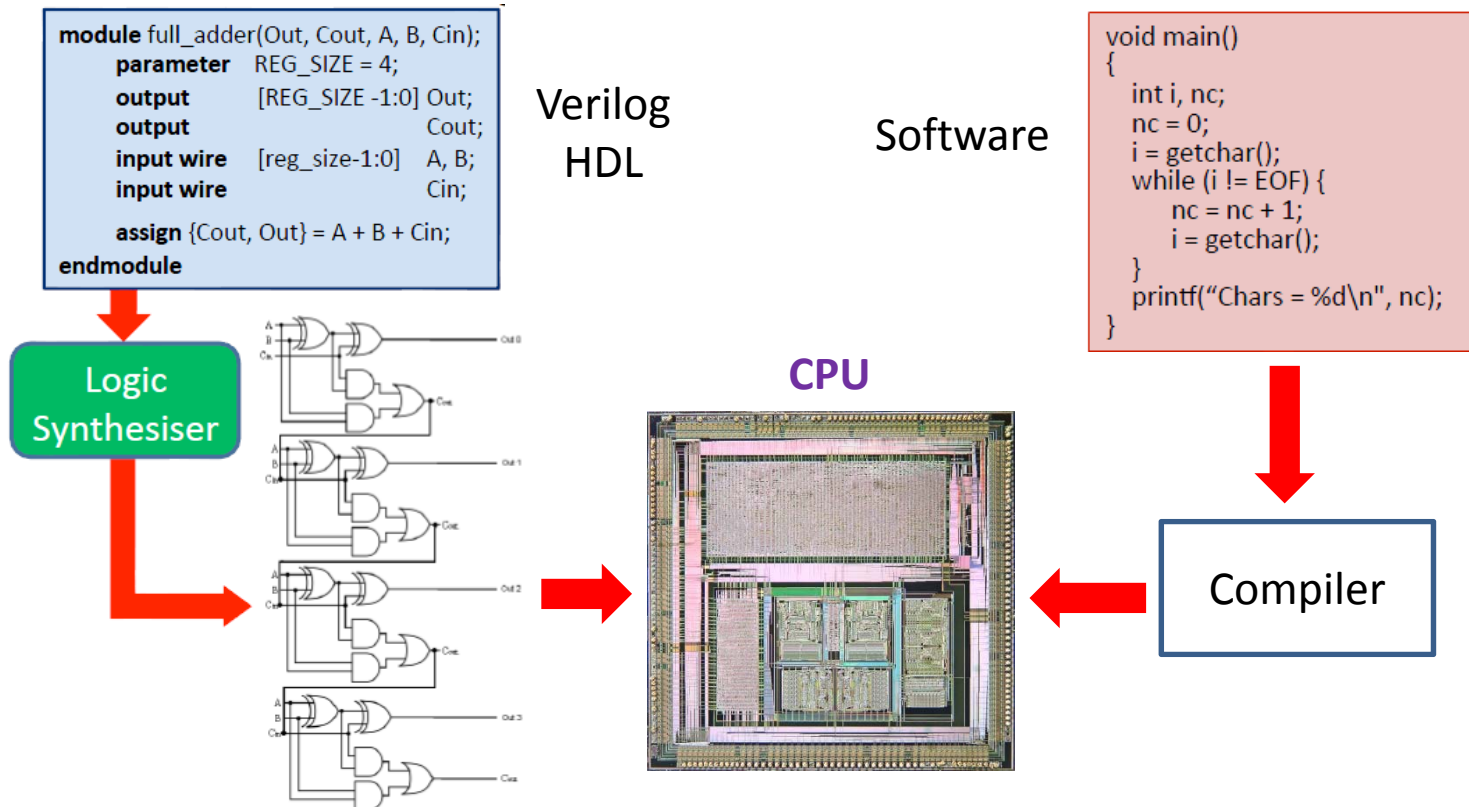
- HDLs are **programming-like** languages that are used to describe hardware
- HDLs are synthesized (and optimized) to hardware primitives
 - **Note: Software is compiled to primitive instructions**



MODULES

Module

- In Verilog, designs are broken down into **modules**
- A **module** is a **container** the designer can use to **encapsulate** a unit of functionality
- Modules can contain code to describe hardware and also instances of other modules
- Good designs consist of sufficient (but not excessive) **levels of hierarchy**, with modules containing instances of modules, that contain instances of other modules
- At each level in the hierarchy, a module instance is treated as a “black-box” – the internals are unknown

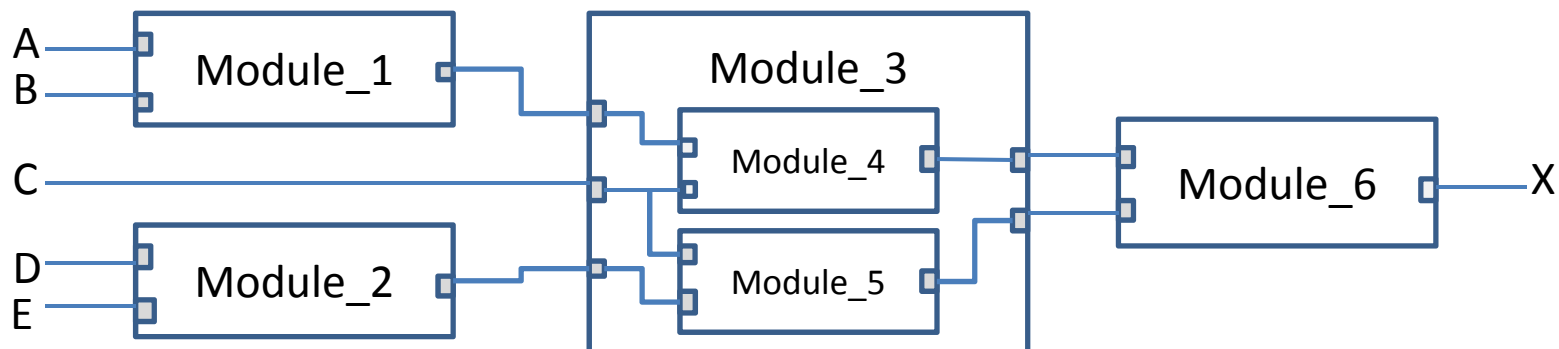

Verilog Module Declaration

- We declare a module in Verilog using the **module** keyword and a list of ports:


```
module somename (port1, port2, port3);
```

- The above declaration describes a module with three **ports**, each a single wire
- We can indicate the direction of the ports using the keywords **input** and **output**:

```
module somename (input port1, port2,  
                 output port3);
```

- The above describes a module with two inputs and one output

Verilog Module Declaration

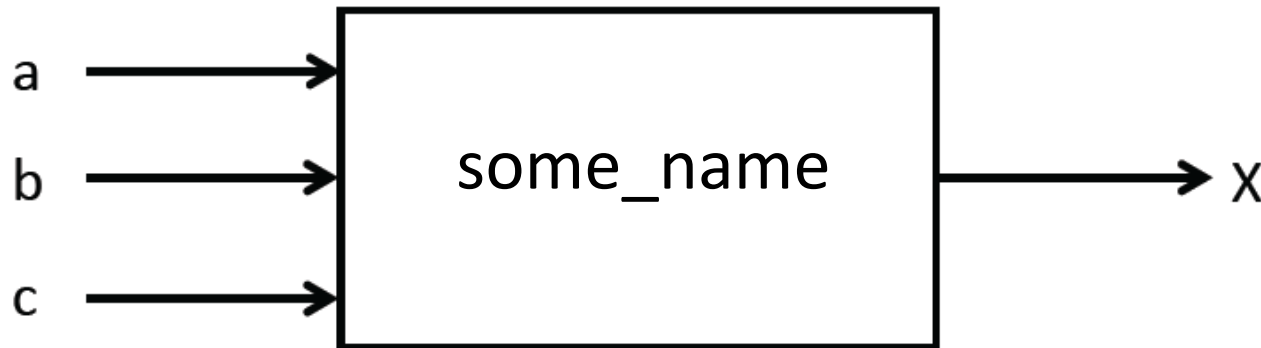

```
module some_name (  
    input a, b, c,  
    output X);  
  
    // Describe your circuit here  
  
endmodule
```


- The **endmodule** keyword indicates the end of statements that comprise the module description

Structural Design using Verilog

- Our first experience with Verilog will be for **structural design**
- This allows us to **structurally** describe any circuit we might otherwise use a circuit diagram for
- The principles learnt in the first half of the course allow us to describe any circuit in terms of these gates

X	Y	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth table for
Full Adder

 

$$S = X \oplus Y \oplus C_i$$

$$C_o = X.Y + X.C_i + Y.C_i$$

Minimize using Boolean
Algebra or K-Maps




```
module full_adder (
    input X, Y, Ci,
    output S, Co);

    // Describe your structural
    // design for full adder here

endmodule
```

Structural Design using Verilog

 - Describing a circuit by its internal structure
- To do this, we need:
 - A module definition – *done*
 - Some gates
 - Wires to connect those gates




We are trying to ‘draw’ the circuit using codes

INSTANTIATING GATE-LEVEL PRIMITIVES

Gate-Level Primitives


- Verilog provides us with basic *primitives* to model Boolean gates: **and**, **nand**, **or**, **nor**, **not**, **xor**, **xnor**

```
and (y, a, b);
```

 

- Represents an **and** gate with inputs connected to wires a and b, and output connected to wire y
- Gate primitives allow more than two inputs:

```
or (z, a, b, c, d);
```

 


- This represents an **or** gate with inputs a, b, and c, d and output z

The (single) output is always the first argument

Verilog Module with Gate Level Primitives

- A simple module that contains just a two-input **and** gate would be written like this:
 
```
module simple_AND (  
    input in1, in2,  
    output out);  
    and (out, in1, in2);  
endmodule
```



- The module's ports act the same as wires (but you **cannot** connect the output of a gate to an input port!)

Of course, we wouldn't create a module for a single *and* gate since the primitive already exists

Wires

- We can declare *internal wires* in a module, using the **wire** keyword:


```
wire int_signal;
```

int_signal

- This creates a named (1-bit) wire that can be used to connect gates together
 - Note: we will see later that it is not always necessary to declare 1-bit wires

Verilog Module with Gate Level Primitives

 
- Let us consider an **and-or-inverter**
- Boolean equation: $out = ((a \bullet b) + (c \bullet d))'$



```
module andorinv (input a, b, c, d,  
                 output out);  
  
    wire and1out, and2out;  
  
    and (and1out, a, b);  
    and (and2out, c, d);  
    nor (out, and1out, and2out);  
  
endmodule
```

Verilog Module with Gate Level Primitives

 - Note you can also use of a unique *identifier* for each gate (this can help in testing):



Gate
Identifiers

```
module andorinv (input a, b, c, d,
                  output out);

    wire and1out, and2out;


    and g1 (and1out, a, b);
    and g2 (and2out, c, d);
    nor g3 (out, and1out, and2out);

endmodule
```

Verilog Module with Gate Level Primitives

- When declaring module ports of the same type and direction, no need for separate declarations, can just use a comma between names:

 
```
module hmm (input in1,  
            input in2,  
            input in3,  
            output out);
```



```
module hmm (input in1,  
            in2, in3,  
            output out);
```

- Also, when declaring multiple wires of the same type, there is no need for separate declarations, use a comma between names:
 
```
wire red;  
wire blue;  
wire green;
```




```
wire red, blue, green;
```

Example: Half Adder in Verilog

- Lets re-look at the binary adder
- A **half-adder** takes two 1-bit inputs and produces a 1-bit **sum** output and a 1-bit carry out (**cout**)
- We can see that **sum** is just an **xor** function and **cout** is just an **and** function

a	b	sum	cout
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 


```
module add_half (  
    input a, b,  
    output sum, cout);  
  
    xor g1 (sum, a, b);  
    and g2 (cout, a, b);  
endmodule
```

Note: g1 and g2 are gate identifiers

 Exercise

- Implement a Verilog module using structural gate-level primitives for the following circuit:




```
module simple_circ (input A, B, C, D, output Y);
    wire int1, int2, int3, int4;

    and (Y, int1, int2);
    not (int1, int3);
    or (int3, A, D);
    and (int2, B, C, int4);
    not (int4, D);

endmodule
```

 Exercise

- Implement a Verilog module using structural gate-level primitives for the following circuit:



```
module simple_circ (input A, B, C, D,
                    output Y);
    wire int1, int2, int3, int4;

    and (Y, int1, int2);
    not (int1, int3);
    or (int3, A, D);
    and (int2, B, C, int4);
    not (int4, D);
endmodule
```


```
module simple_circ (input A, B, C, D,
                    output Y);
    wire int1, int2, int3, int4;

    not (int1, int3);
    not (int4, D);
    and (int2, B, C, int4);
    and (Y, int1, int2);
    or (int3, A, D);
endmodule
```

These two implementations will produce the same circuit

Verilog Module with Gate Level Primitives

 - Note that the **order** of statements is **unimportant**
- Each statement describes a piece of hardware
- There is no sequence of steps when doing structural Verilog
- Usually we declare internal signals first, and then instantiate gates



A Note on Wires

- There is no need to declare 1-bit wires for connecting modules
- Tools will infer these wires automatically by matching names
- But **only** for 1-bit wires in instantiation:

```
module simple_circ (input A, B, C, D,  
                   output Y);  
  
    wire int1, int2, int3, int4;  
  
    and (Y, int1, int2);  
    not (int1, int3);  
    or  (int3, A, D);  
    and (int2, B, C, int4);  
    not (int4, D);  
endmodule
```

```
module simple_circ (input A, B, C, D,  
                   output Y);  
  
    and (Y, int1, int2);  
    not (int1, int3);  
    or  (int3, A, D);  
    and (int2, B, C, int4);  
    not (int4, D);  
endmodule
```

So, instead of this:

This is OK!

Additional Notes

- Verilog is **case-sensitive!**
 - FIFO_out, fifo_out and Fifo_Out refer to different things
- Statements are terminated with a semi-colon (;)
- Comments are **C-style**:
 - // starts a single line comment
 - /* is used for block comments */ – cannot be nested!
- Whitespace is ignored – But you **should** use it to make your code readable
- **Identifiers** in Verilog:
 - Must start with a **letter** or **underscore** (_)
 - Can contain **letters, numbers, underscore**, and **dollar** (\$)
 - Must not clash with keywords (e.g. **module** , **input**, etc.)

```
module and_or_inv (input a, b, c, d,
                  output out);


    wire and1out, and2out;

    and g1 (and1out, a, b); // AND gate
    and    g2 (and2out, c, d);
    nor g3 (out, and1out,    // NOR gate
           and2out);

endmodule
```


MODULE INSTANTIATION

Half Adder and Full Adder

 

```
module add_half (  
    input a, b,  
    output sum, Cout);  
  
    xor g1 (sum, a, b);  
    and g2 (Cout, a, b);  
endmodule
```

 A **full adder** can be implemented using 2 Half-Adders and an OR gate (see slides on Digital Arithmetic)





```
module full_add (input A, B, Cin  
                output sum, Cout);  
    wire w1, w2, w3;  
  
    xor g1 (w1, A, B);  
    and g2 (w2, A, B);  
    xor g3 (sum, Cin, w1);  
    and g4 (w3, Cin, w1);  
    or g5 (Cout, w2, w3);  
endmodule
```

This is tedious!



Instantiation in Verilog

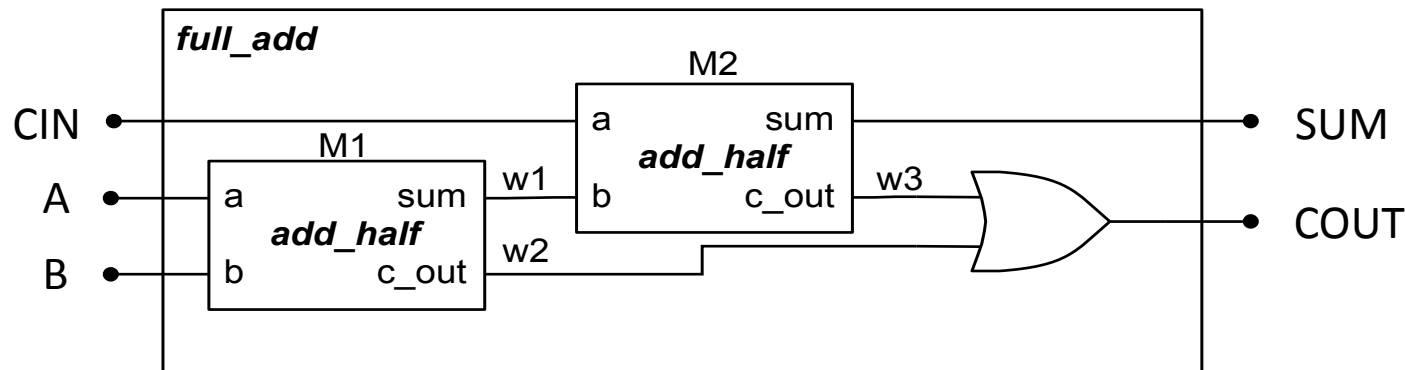 - In Verilog, we can use existing modules within new modules through **instantiation**
- For example, we can **instantiate** the half adder module we previously designed **within** a new module



Instantiation in Verilog (Full Adder)
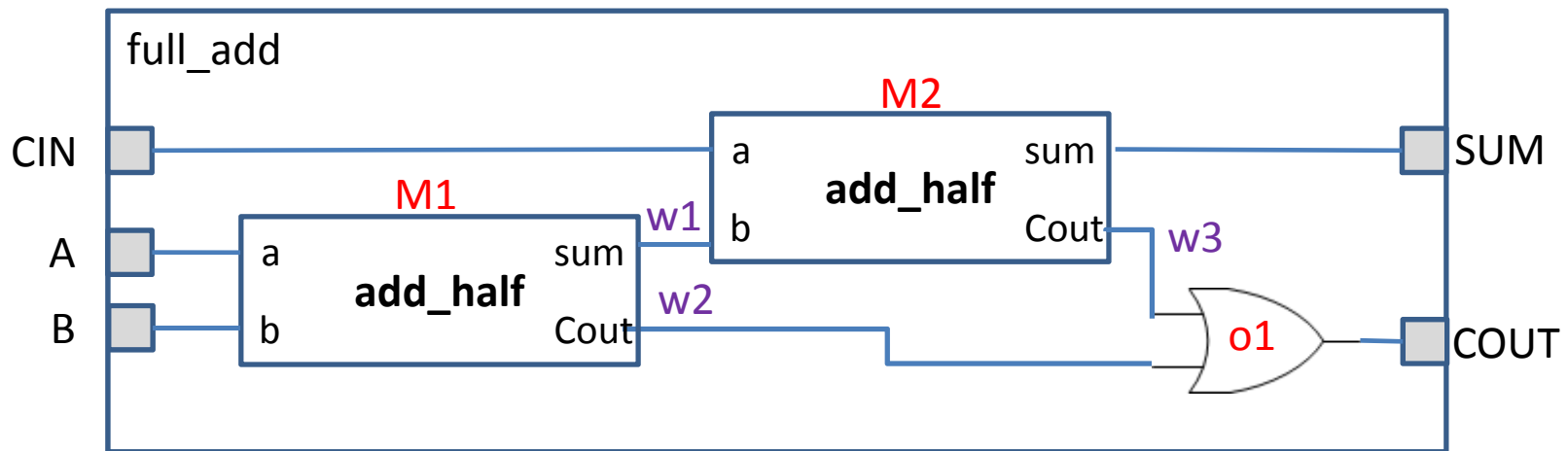 
```
module add_half (input a, b,  
                 output sum, Cout);  
    xor g1 (sum, a, b);  
    and g2 (Cout, a, b);  
endmodule
```




```
module full_add (input A, B, CIN,  
                output SUM, COUT);  
    wire w1, w2, w3;  
  
    add_half M1 (A, B, w1, w2);  
    add_half M2 (CIN, w1, SUM, w3);  
    or o1 (COUT, w3, w2);  
endmodule
```

Instantiation in Verilog

- We *instantiate* a module by invoking its name and giving an *instance* a name:



```
add_half M1 (A, B, w1, w2);
```

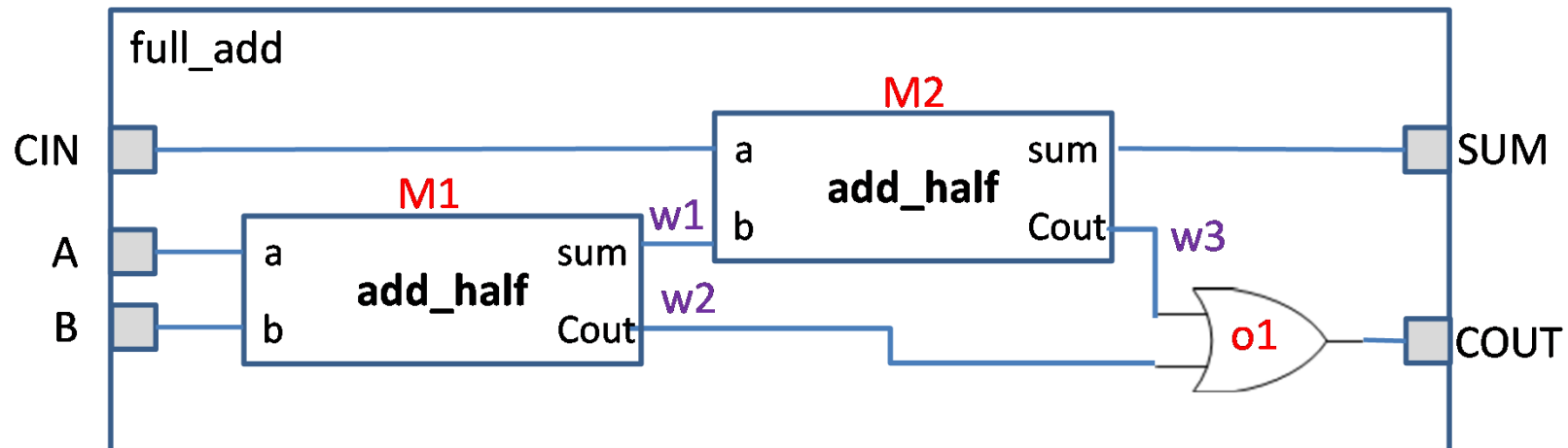- Creates an *instance* called **M1** of module **add_half**
- It then **connects the signals and ports** referenced in the parentheses with the corresponding ports of the instantiated module
 - Just like we did previously with gate-level primitives



Ordered Instantiation

- The **order** determines connections
- Looking at the original **add_half** module declaration:
- Its first port is its **a** input, the second its **b** input, the third its **sum** output and the fourth its **Cout** output
- Connects a wire called **A** in the outer module with the **a** port, **B** with the **b** port, the **w1** wire to its **sum** output and the **w2** wire to its **Cout** port

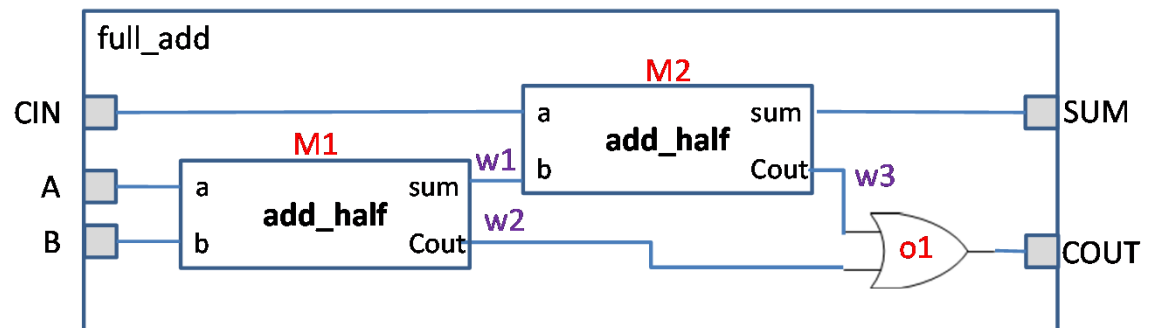 

```
module add_half (input a, b,  
                 output sum, Cout);  
    xor g1 (sum, a, b);  
    and g2 (Cout, a, b);  
endmodule
```

```
add_half M1 (A, B, w1, w2);
```

```
add_half M2 (CIN, w1, SUM, w3);
```

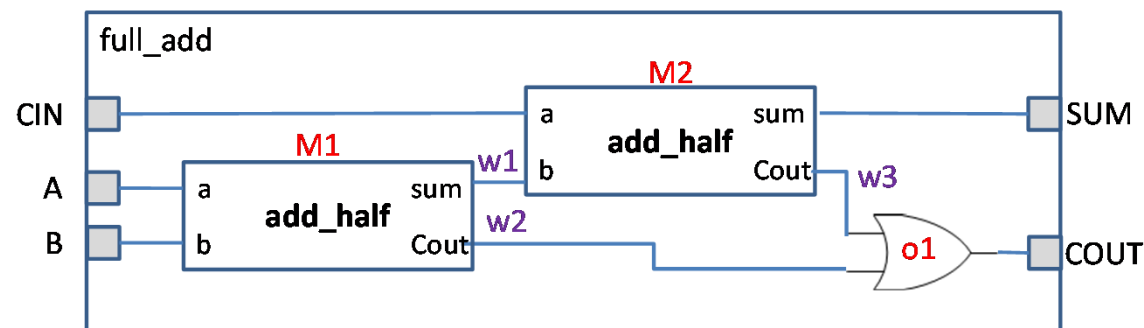

Named Instantiation

- Connecting instantiated modules to wires and ports in the manner just described can be **error-prone**:
 - Must remember the order of the ports
 - If we change the port order or add/remove ports, we have to change the instantiation
- Hence, we generally use a ***named connection***:

```
add_half M1 (.a(A),  
             .b(B),  
             .sum(w1),  
             .Cout(w2));
```

```
add_half M2 (.a(CIN),  
             .b(w1),  
             .sum(SUM),  
             .Cout(w3));
```

The port name is preceded by a dot, and the connected signal is placed in the brackets



Instantiation in Verilog


Ordered Instantiation

```
module full_add (input A, B, CIN,
                 output SUM, COUT);
    wire w1, w2, w3;

    add_half M1 (A, B, w1, w2);
    add_half M2 (CIN, w1, SUM, w3);
    or O1 (COUT, w3, w2);

endmodule

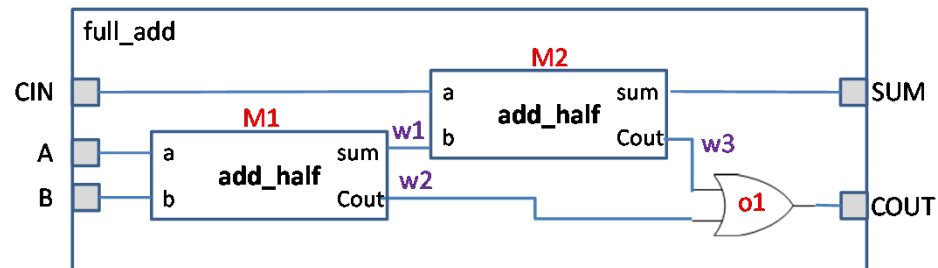module add_half (input a, b,
                 output sum, Cout);
    xor G1 (sum, a, b);
    and G2 (Cout, a, b);
endmodule
```



Named Instantiation

```
module full_add (input A, B, CIN,
                 output SUM, COUT);
    wire w1, w2, w3;

    add_half M1 (.a(A), .b(B),
                .sum(w1),
                .Cout(w2));

    add_half M2 (.a(CIN), .b(w1),
                .sum(SUM),
                .Cout(w3));

    or O1 (COUT, w3, w2);
endmodule

module add_half (input a, b,
                 output sum, Cout);
    xor G1 (sum, a, b);
    and G2 (Cout, a, b);
endmodule
```

 

VERILOG ASSIGNMENTS

Verilog Assignments

- Implementing larger circuits using individual gates can be tedious.

Instantiating
gate primitive


```
and (y, a, b);
```



- Verilog allows us to use combinational logic **expressions** through the **assign** keyword:

Continuous
assignment

```
assign y = a & b;
```

 

- This is called a **continuous assignment**
 - As it is always permanently assigned
- It allows us to assign the result of a Boolean expression to a signal

This is much simpler than using gate primitives

Verilog Assignments


- We can use a range of operators:

- **&&** : and (bitwise is: **&**)
- **||** : or (bitwise is: **|**)
- **!** : not (bitwise is: **~**)
- **^** : xor (bitwise is: **^**)

Operator	Name
~	Bitwise NOT
&	Bitwise AND
	Bitwise OR
^	Bitwise XOR
~&	Bitwise NAND
~	Bitwise NOR

- The and-or-inverter example previously shown:

 - The ***assign statement*** allows the use of more complex operators and operands – more on this later



Instantiating
gate
primitives


```
wire and1out, and2out;
nor g3 (out, and1out, and2out);
and g2 (and2out, c, d);
and g1 (and1out, a, b);
```

```
assign out = ~((a&b) | (c&d));
```

Continuous
assignment

Continuous Assignment Example

- Full Adder (using assign statements)

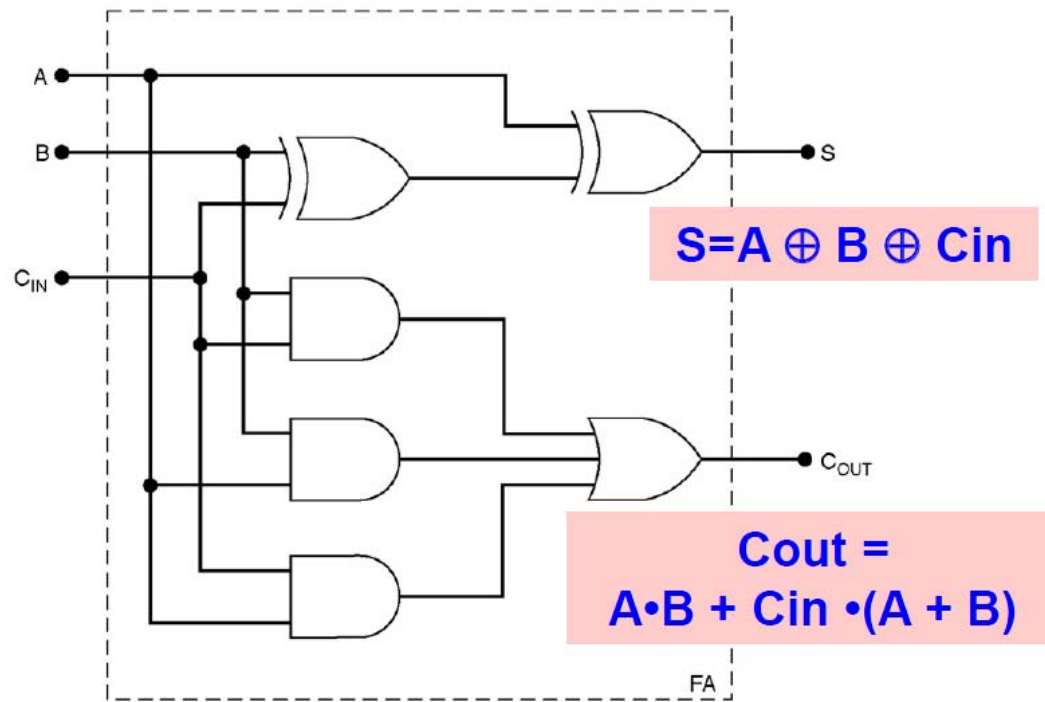


Remember that all
assign statements
happen
concurrently (at
the same time)

```
module full_adder (input A, B, Cin,  
                  output S, Cout);  
  
    assign S      = A ^ B ^ Cin;  
    assign Cout = (A & B) | (B & Cin) | (A & Cin);  
  
endmodule
```

 
Exercise

- You should now be able to go from circuit to structural Verilog description, or assign statement, and vice versa.
- Try this (use a single assign statement):



```
assign f = (~a | (b&c)) ^ ((b&c) ~| d);
```

Conditional Assignment

- We have already seen the continuous assignment statement:


```
assign y = ~((a & b) | (c & d));
```

- It is also possible to have a conditional assignment (as in C):

```
assign y = sel ? x1 : x0; // a multiplexer
```

The signal **y** will be connected to **x1** if **sel** is 1, else it is connected to **x0**

1-bit 2x1 mux

 

Basic Combinational Arithmetic

- We will not cover the details of arithmetic in Verilog in the course, but a few things are worth knowing
- Verilog supports many basic *arithmetic operations*:
 - Arithmetic: $+$, $-$, $*$, $/$ (division is not generally synthesizable)
 - Comparisons: $<$, $<=$, $>$, $>=$, $==$, $!=$
 - The comparisons are evaluated as true (1) or false (0)
- These can be useful in statements like these:

```
assign sum = a + b;  
assign diffval = curr - prev;  
assign max = (a>b) ? a : b;
```

VECTORS IN VERILOG

So far we have used 1-bit signals

- What happens if I want to use multi-bit signals
 - After all it is very difficult do anything with 1 binary bit
- Verilog has a special construct for handling multi-bit signals (wires). **Formed by specifying a range:**

```
wire [31:0] databus;
```

- Also for specifying multi-bit module ports

```
module add16 (input [15:0] a, b,
              output [15:0] sum,
              output cout);

    // add module internals here

endmodule
```

$\overline{\text{32}}$ databus

is short
for
↓

— databus[31]
— databus[30]
—
— databus[0]

Vectors in Verilog

- We can declare *multi-bit* signals (or busses as we have seen them called) in Verilog:

```
..., output [3:0] y, ...  
wire [7:0] something;
```

- By convention, we label the *most significant bit* (MSB) using the higher number, and the *least significant bit* (LSB) using zero
- So a *16-bit* signal will be [15:0], an *8-bit* signal will be [7:0], and a *64-bit* signal will be [63:0]

Example: Adder

- Consider the 32-bit adder below (with Carry in & out)

```
module adder (  
    input Cin,  
    input [31:0] A, B,  
    output Cout,  
    output [31:0] Sum);  
  
    wire [32:0] w1;  
  
    assign w1    = A + B + Cin;  
    assign Sum   = w1[31:0];  
    assign Cout  = w1[32];  
  
endmodule
```

- We must declare multi-bit signals

Vectors in Verilog

- *Vectors* are really easy to work with
- We can select *individual bits* of the vector:

```
assign y = some[3]; //assign 4th bit of  
                  //some to y
```

- We can select a *range* of the vector:

```
assign z = some[4:3]; //assign 5th/4th bit of some  
                    //to two-bit signal z
```

- We can *assign* to individual bits or a range:

```
assign x[0] = y[1];  
assign x[2:1] = y[4:3];
```


Vectors in Verilog

- But be careful! Widths of vectors in assignments *should match*.
- Verilog will let you do some really bad things:
 - Like in the previous example, **so be VERY careful!!!!**

```
assign x[2:0] = y[1];  
assign x[2:1] = a;    // a 1-bit
```

- With arithmetic, this can be **catastrophic!**
- Always check you are assigning signals of equal width, and remember **the LSB index is zero!**

Always carefully check the Synthesis warnings!

Number Literals

- What about assigning a fixed bit pattern to a signal?
- Verilog allows us to use number *literals*:
 - `<size>'<radix><value>`
 - `<size>` is the width **in bits**
 - `<radix>`: b for binary, o for octal, h for hex, d for decimal
 - `<value>`: the number you want, with as many optional underscores as needed (for readability)
- Examples:
 - `4'b0000` (4 binary bits “0 0 0 0”)
 - `8'h4F` (= `8'b01001111`)
 - `8'b0100_1111` (Same as above. Note the use of the underscore)
 - `1'b1` (a single “1”)

Number Literals

- Underscores can help split long strings:
 - 16'b0010_1110_0110_1001 (easier than 0010111001101001)
 - In this example, it's better to use hex instead (16'h2E69)
 - 32'h0F4B_C009
- If you assign a literal to a larger signal, it is *zero-padded at the MSB*:


```
wire [5:0] x = 4'b1001 //x=001001
```

- If you assign a literal to a smaller signal, it is *truncated at the MSB*:

```
wire [3:0] x = 6'b110011 //x=0011
```

Concatenation

 - It is sometime very useful to be able to concatenate a number of signals into a single signal.
 - Concatenation is signified by curly brackets enclosing a list



```
wire [3:0] a, b;  
wire [7:0] y;  
...  
assign y = {a, b};
```

Concatenation and Replication

- Concatenation

```
assign b = {a[3:0], 4'b0000}; // b is 8 bit
```

- Replication uses braces with a preceding integer or variable representing an integer.

```
assign c = {{4{a[3]}}}, a[3:0]}; // c is 8-bit
```

- The above example replicates the most significant bit 4 times

PARAMETERS

Parameters

- A **parameter** is a constant that is local to a module
 - Can be declared in the module header
 - Can also be declared in the module body (we will not use this)

```
module some_mod #(parameter SIZE=8) (  
    input    [SIZE-1:0] X, Y,  
    output [SIZE-1:0] Z);
```

- Can have multiple parameters

```
module some_mod #(parameter SIZE=8, WIDTH=16)(  
    input    [SIZE-1:0] X, Y,  
    output [WIDTH-1:0] Z);
```


Parameters

- It is also possible to redefine a **parameter**
 - Consider the following 8-bit module

```
module submod #(parameter SIZE=8) (  
    input  [SIZE-1:0] X, Y, output [SIZE-1:0] Z;  
    // some statements in here  
endmodule
```

- Then, note the change in the parameter in the submodule instantiation below
 - Now using two 16-bit submodules

```
module top_mod #(parameter SIZE=16) (  
    input  [SIZE-1:0] a, b, c, output [SIZE-1:0] D, E);  
  
    submod #(.SIZE(SIZE)) U1 (.X(a), .Y(b), .Z(D));  
    submod #(.SIZE(SIZE)) U2 (.X(c), .Y(b), .Z(E));  
  
endmodule
```

In practice, it may be better to call them different names to avoid confusion

Example: Adder

- Consider the 32-bit adder below (with Carry in & out)

```
module adder #(parameter SIZE=32)(  
    input Cin,  
    input [SIZE-1:0] A, B,  
    output Cout,  
    output [SIZE-1:0] Sum);  
  
    assign {Cout, Sum} = A+B+Cin;  
  
endmodule
```

- Note:**
1. How the concatenation operator handles the 33-bit result produced by $A+B+Cin$
 2. The use of the arithmetic addition operator (+) to generate the sum.

